

## Seventh Semester B.E. Degree Examination, June/July 2016 Computer Techniques in Power System Analysis

Time: 3 hrs.

Max. Marks:100

**Note: Answer FIVE full questions, selecting at least TWO questions from each part.**

### PART - A

- 1 a. Explain the terms: (i) Tree (ii) Co-Tree (iii) Tree branch path incidence matrix with an example. (10 Marks)
- b. For the power system shown below. Select ground as reference and a tree for which the link elements are 1 - 2, 1 - 4, 2 - 3 and 3 - 4. Write the basic cut set and basic loop incidence matrix. Verify the relation  $C_b = -B_l^T$  (10 Marks)

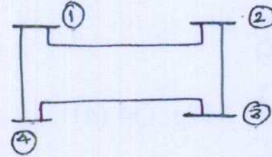


Fig. Q1(b)

- 2 a. Consider the power system network shown below:

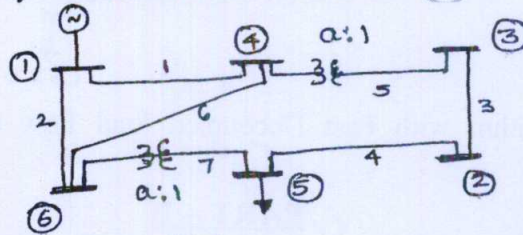


Fig. Q2 (a)

The data is given below:

| Line No. | Between lines | Line impedance   | $\frac{y'_{pq}}{2}$ | Off nominal turns ratio |
|----------|---------------|------------------|---------------------|-------------------------|
| 1        | 1 - 4         | $0.08 + j0.37$   | 0.007               | -                       |
| 2        | 1 - 6         | $0.123 + j0.518$ | 0.010               | -                       |
| 3        | 2 - 3         | $0.723 + j1.05$  | 0                   | -                       |
| 4        | 2 - 5         | $0.282 + j0.64$  | 0                   | -                       |
| 5        | 4 - 3         | $0 + j0.133$     | 0                   | 0.909                   |
| 6        | 4 - 6         | $0.097 + j0.407$ | 0.0076              | -                       |
| 7        | 6 - 5         | $0 + j0.30$      | 0                   | 0.976                   |

A static shunt capacitor is connected at bus 4 with the admittance  $j0.005$  pu. Formulate  $Y_{BUS}$  by inspection method. (12 Marks)

- b. Form the  $Z_{BUS}$  for the power system shown below. Select node ① as reference. The line reactances are marked in pu. (08 Marks)


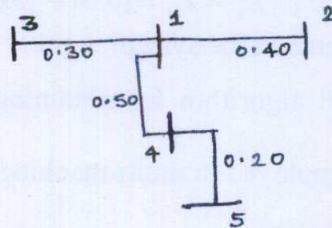


Fig. Q2 (b)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

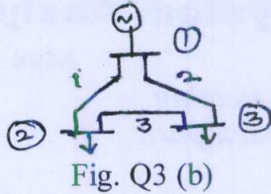- 3 a. Explain with the help of a flow chart Gauss Seidel method of load flow analysis in a power system. (10 Marks)
- b. Compute the line flows and line losses for a 3-Bus power system network shown below. The data obtained from load flow is as follows: (10 Marks)



| Element No. | Bus From To | R    | X     | Bus No. | V       | $\delta$ |
|-------------|-------------|------|-------|---------|---------|----------|
| 1           | 1 - 2       | 0.02 | 0.04  | 1       | 1.05    | 0.0      |
| 2           | 1 - 3       | 0.01 | 0.03  | 2       | 0.9818  | -3.5°    |
| 3           | 2 - 3       | 0.02 | 0.025 | 3       | 1.00125 | -2.665°  |

- 4 a. In a two bus system shown in Fig. Q4 (a). The bus 1 is slack bus with  $V = 1.0 \angle 0^\circ$  pu and bus 2 is a load bus with  $P = 100$  MW,  $Q = 50$  MVar. The line impedance is  $(0.12 + j0.16)$  pu on a base of 100 MVA. Using Newton Raphson load flow method compute  $|V_2|$  and  $\delta_2$  upto one iteration. (10 Marks)

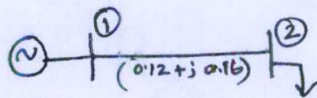


Fig. Q4 (a)

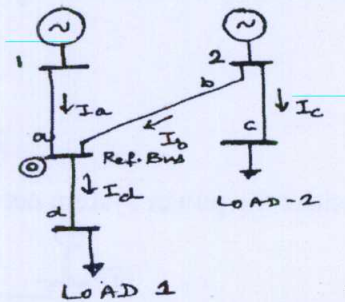


Fig. Q6 (b)

- b. Explain the algorithm with Fast Decoupled load flow analysis, clearly stating all the assumptions made. (10 Marks)

**PART - B**

- 5 a. What is meant by economic load scheduling? Explain the Hydro and Thermal unit input-output curves. (10 Marks)
- b. A power plant has three units with following cost characteristics:  
 $F_1 = 0.05P_1^2 + 21.5P_1 + 800$  Rs./hr;  $F_2 = 0.10P_2^2 + 27P_2 + 500$  Rs./hr  
 $F_3 = 0.07P_3^2 + 16P_3 + 900$  Rs./hr  
 Find the optimum scheduling and total cost in Rs./hr for a total load demand of 200 MW. Given that  $P_{i,max} = 120$  MW:  $P_{i,min} = 39$  MW: where  $i = 1, 2, 3$ . (10 Marks)

- 6 a. Explain optimal scheduling of hydro-thermal plants and also explain its problem formulation. (10 Marks)
- b. Figure shown in Fig.Q6(b) is having two plants 1 and 2 which are connected to the buses 1 and 2 respectively. There are two loads and 4 branches. The reference bus with a voltage of  $1.0 \angle 0^\circ$  pu is shown in the diagram. The branch currents and impedances are as follows:  
 $I_a = (2 - j0.5)$ pu;  $I_b = (1.6 - j0.4)$ pu;  $I_c = (1 - j0.25)$ pu;  $I_d = (3.6 - j0.9)$ pu;  
 $Z_a = Z_b = (0.015 + j0.06)$ pu;  $Z_c = Z_d = (0.01 + j0.04)$ pu  
 Calculate the loss coefficients in the system in pu. (10 Marks)

- 7 a. Explain the computational algorithm for obtaining the swing curves using Runge Kutta method. (10 Marks)
- b. Explain the load models employed in multi-machine stability analysis with neat sketch. (10 Marks)
- 8 a. Explain Milne's predictor corrector method for solving the swing equation of multi-machine system. (10 Marks)
- b. Explain the swing equation and its importance in stability studies. (10 Marks)

\*\*\*\*\*