

CRASH COURSE

USN

--	--	--	--	--	--	--	--	--	--

10EE751

Seventh Semester B.E. Degree Examination, May 2017 H.V.D.C. Transmission

Time: 3 hrs.

Max. Marks: 100

Note: Answer FIVE full questions, selecting at least TWO questions from each part.

PART – A

- 1 a. Describe the historical sketch of HVDC transmission. (08 Marks)
b. With relevant figures, explain the types of DC links and HVDC converter station. (12 Marks)
- 2 a. Explain the constitution of EHV-AC and DC links. (12 Marks)
b. Mention the applications and advantages of HVDC transmission. (08 Marks)
- 3 a. Define pulse number and explain the concept of pulse number. (08 Marks)
b. Explain three phase bridge rectifier circuit with relevant waveforms. (12 Marks)
- 4 a. What are the assumptions made in converter circuits? (03 Marks)
b. Mention the “choice of best circuit for HVDC converters” and its advantages. (07 Marks)
c. Compare single phase full wave and single phase bridge circuit with respect to currents, voltages, VA, number of valves. (10 Marks)

PART – B

- 5 a. A graetz bridge operates with a delay angle of 15° . The leakage reactance of the transformer is 10Ω . The line to line AC voltage is 85kV. Compute the overlap angle and DC voltage for i) $I_d = 2000A$; ii) $I_d = 4500A$. (12 Marks)
b. Describe the complete characteristics of rectifier. (08 Marks)
- 6 a. Explain the form of grid pulse. (08 Marks)
b. Describe the desired features of control. (04 Marks)
c. Describe the schematic diagram of constant current regulator. (08 Marks)
- 7 a. What are the drawbacks of IPC and EPC schemes? (06 Marks)
b. Describe the actual control characteristics and combined characteristics of rectifier and inverter. (14 Marks)
- 8 a. Explain the purposes of DC reactors. (04 Marks)
b. Explain in detail of current oscillations and anode dampers. (12 Marks)
c. Explain Re-energization of d. c. line. (04 Marks)

* * * * *