

USN

--	--	--	--	--	--	--	--	--	--

10EE751

Seventh Semester B.E. Degree Examination, Dec.2017/Jan.2018
HVDC Transmission

Time: 3 hrs.

Max. Marks:100

Note: Answer any FIVE full questions, selecting atleast TWO questions from each part.

PART – A

- 1 a. With relevant figure, explain the constitution of EHV-AC and DC links. (10 Marks)
b. With a neat diagram, explain different kinds of DC links. Explain the necessity of back – to –back HVDC link. (10 Marks)
- 2 a. Summarize the advantages and disadvantages of HVDC transmission system. (08 Marks)
b. Compare HVAC and HVDC transmission for economic of operation, stability limit and reactive power limit. (12 Marks)
- 3 a. Draw the schematic diagram of a typical HVDC converter station and explain the function of each component. (08 Marks)
b. Explain the three – phase one-way rectifier circuit with wave form and obtain.
 - i) Average direct voltage
 - ii) Peak – to –peak ripple
 - iii) PIV
 - iv) Aggregate valve rating
 - v) VA rating of transformer primary and secondary. (12 Marks)
- 4 a. Explain the three – phase two-way rectifier (Graetz bridge) circuit with waveform and obtain:
 - i) Average direct voltage
 - ii) Peak – to –peak ripple
 - iii) PIV
 - iv) Aggregate valve rating
 - v) VA rating of transformer primary and secondary. (12 Marks)
b. 'Best converter circuit for the HVDC transmission is 3-phase bridge. Justify the statement by explain advantages of a 3-phase graetz bridge configuration. (08 Marks)

PART – B

- 5 a. With relevant figures and waveforms, derive the expression for average DC output voltage of the bridge converter without overlap. Assume converter firing angle as α . Also obtain the relation between $\cos \phi$ and $\cos \alpha$. (10 Marks)
b. With relevant waveform, derive an expression for average DC voltage in a bridge converter with an overlap of less than 60 degrees. (10 Marks)
- 6 a. Explain the basic means of control. (05 Marks)
b. Explain the limitations of manual control. (05 Marks)
c. Discuss constant current verses constant voltage alternatives for a DC transmission system. (05 Marks)
d. What are the desired features of control of DC lines? (05 Marks)

- 7 a. Describe the actual control characteristics. (08 Marks)
 b. Explain and draw the schematic circuit of analog computer for C.E.A (Current – Excitation- Angle) control with voltage waveform. (12 Marks)
- 8 a. Describe the current oscillations and anode dampers. (10 Marks)
 b. The following data pertain to a certain converter :
- | | | |
|--------------------------------|----------|----------------------------|
| Commutating voltage | = E_c | = 113KV rms phase to phase |
| Stray capacitance across valve | = C | = 100pF |
| Stray inductance of the valve | = L | = 100 μ H |
| Excitation current | = 50A | |
| Commutating inductance | = $2L_c$ | = 42.2mH phase to phase |
- stray resistance is assumed to be negligible
- Find the undamped natural frequency and amplitude of the oscillation of current in the incoming valve at the beginning of commutation under the most severe condition. (10 Marks)