

USN

--	--	--	--	--	--	--	--	--	--

10EE751

**Seventh Semester B.E. Degree Examination, June/July 2019**  
**HVDC Transmission**

Time: 3 hrs.

Max. Marks: 100

**Note: Answer any FIVE full questions, selecting at least TWO questions from each part.**

**PART – A**

- 1 a. With suitable schematics, explain the constitution of EHV AC and DC lines. (10 Marks)
- b. i) List any four advantages and disadvantages of HVDC transmission system. (10 Marks)
- ii) Mention any two applications of HVDC transmission. (10 Marks)
- 2 a. Compare the HVAC and HVDC transmission for economics of operation, stability limit, voltage control and reliability. (12 Marks)
- b. With a neat diagram, explain the different kinds of HVDC links. (08 Marks)
- 3 a. What are the assumptions made while studying the properties of converter circuits? (03 Marks)
- b. Explain the six-phase diametrical rectifier circuit. (05 Marks)
- c. Describe the  $1 - \phi$  full wave rectifier with waveform and obtain the PIV, pulse number, average value of voltage, aggregate VA rating of valves. (12 Marks)
- 4 a. Explain the three phase one way rectifier circuit with waveform and obtain
  - i) Average direct voltage
  - ii) PIV
  - iii) Aggregate VA rating of valves
  - iv) VA rating of transformer primary and secondary winding. (12 Marks)
- b. "Best converter circuit for the HVDC transmission is 3 phase bridge". Justify the statement by explaining the advantages of a 3-phase bridge configuration. (08 Marks)

**PART – B**

- 5 a. With relevant figures and waveforms, explain the operation of Graetz bridge circuit. Derive the expression for average DC output voltage of converter without overlap. (10 Marks)
- b. Derive the expression for average direct voltage of a six pulse converter with a delay angle of ' $\alpha$ ' and overlap angle of less than  $60^\circ$ . (10 Marks)
- 6 a. Draw the electrical equivalent circuit of a HVDC link and explain the basic principles of controlling the voltage of any point on the line and the current. Also explain the reversal of power. (10 Marks)
- b. Discuss the actual control characteristics of converter. In this context, explain the significance of current margin and its ranges. (10 Marks)
- 7 a. Explain the stability of control as considering a damping circuit. (10 Marks)
- b. Explain the constant current control in HVDC converter stations. (10 Marks)
- 8 a. Enumerate the functions of smoothing reactor in case of HVDC transmission systems. (06 Marks)
- b. Explain the causes of oscillations on DC lines. (06 Marks)
- c. Explain how current oscillations are minimized using anode dampers. (08 Marks)

\* \* \* \* \*

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.