

Reg. No.

--	--	--	--	--	--	--	--	--	--

Seventh Semester B.E. Degree Examination, January/February 2006
Electrical & Electronics Engineering
High Voltage Engineering

Time: 3 hrs.)

(Max.Marks : 100)

Note: Answer any FIVE full questions.

1. (a) List the advantages of very high voltages for transmission purposes. What is the highest value of AC transmission voltage in India? What is the need for generating high voltages in laboratory? (10 Marks)
- (b) Explain any three ionisation processes taking place in a gas. (10 Marks)
2. (a) Explain Townsend's theory of breakdown of gases. Derive the current growth equation. (12 Marks)
- (b) In an experiment in a certain gas it was found that the steady state current is 5.5×10^{-8} A at 8 KV at a distance of 0.4cm between the plane electrodes. Keeping the field constant and reducing the distance to 0.1 cm results in a current of 5.5×10^{-9} A. Calculate Townsend's primary ionisation coefficient α . (4 Marks)
- (c) Derive Paschev's law. (4 Marks)
3. (a) Explain the suspended particle theory and the stressed oil volume theory of breakdown in liquids. (10 Marks)
- (b) Explain the electromechanical breakdown and thermal breakdown of solid dielectrics. (10 Marks)
4. (a) With a neat diagram explain the two stage cascade transformer connection to produce high voltages at 50 Hz. (8 Marks)
- (b) A 100KV A, 400V/250V testing transformer has 8% leakage reactance and 2% resistance on 100kVA base. A cable has to be tested at 500kV using the above transformer as a resonant transformer at 50Hz. If the charging current of the cable at 500kV is 0.4A, find the series inductance required. Assume 2% resistance for the inductor to be used and the connecting leads. Neglect the dielectric loss of the cable. What will be the input voltage to the transformer? (6 Marks)
- (c) Three 500kV, 500KV A transformers with a short circuit impedance of 12% are connected in cascade. Determine the rated full load current, impedance in ohms and the short circuit currents when the transformers are excited to 350 kV each. (6 Marks)
5. (a) With a neat diagram explain the working of 4 stage Cock roft - Walton DC generator. Derive expressions for ripple and output voltage. (12 Marks)
- (b) An impulse generator has eight stages with each condenser rated for $0.16\mu F$ and 125kV. The load capacitance available is $1000pF$. Find the series resistance and the damping resistance needed to produce $1.2/50\mu s$ impulse wave. What is the maximum output voltage of the generator. If the charging voltage is 120 kV? (8 Marks)

6. (a) With a neat diagram explain the construction and working of an electrostatic voltmeter. What are its advantages and disadvantages ? (10 Marks)
- (b) List the chief sources of errors in potential dividers for impulse voltage measurements. (5 Marks)
- (c) The flashover voltage of an insulator at room temperature and pressure of 18°C and 680mm of mercury pressure is 225kV . Determine the flashover voltage at standard temperature and pressure of 26°C and 760mm of Hg pressure. (5 Marks)
7. (a) Explain the method of measuring high voltages using sphere gaps. Also explain the factors affecting the measurements. (10 Marks)
- (b) Explain the method of measuring the capacitance and $\tan \delta$ of a capacitor using a high voltage Schering Bridge. Derive the relevant equations. (10 Marks)
8. (a) Explain the method of measuring high voltages using an ammeter in series with a high impedance. (5 Marks)
- (b) Write a short note on magnetic links. (5 Marks)
- (c) With neat diagrams explain the impulse testing of transformers. How are the faults detected and located ? (10 Marks)

*** **