

# ONE TIME EXIT SCHEME

USN

--	--	--	--	--	--	--	--	--	--

10EE74

## Seventh Semester B.E. Degree Examination, April 2018 Industrial Drives and Applications

Time: 3 hrs.

Max. Marks:100

**Note:** 1. Answer any FIVE full questions, selecting atleast TWO questions from each part.  
2. Missing data, if any, may be suitably assumed.

### PART – A

- 1 a. What are the advantages of an electric drive? (04 Marks)  
b. Describe three types of power modulators used in electrical drives, with sketch. (06 Marks)  
c. Describe the different components of load torque. (04 Marks)  
d. A horizontal conveyor belt moving at a uniform speed of 1.2m/s transports materials at the rate of 100 tonnes/hr. The belt is 200m long and driven by a motor at 1200rpm  
i) Sketch the system  
ii) Determine the load inertia referred to the motor shaft. (06 Marks)
- 2 a. With suitable sketches, and heating curves describe any four classes of motor duty. (08 Marks)  
b. With usual notations, derive the expression for temperature rise of a machine. Sketch the temperature rise versus time curve. (06 Marks)  
c. A constant speed motor has the following duty cycle :  
i) Load rising linearly from 0 to 200 KW in 4 minutes  
ii) Uniform load 200 KW for 2 minutes  
iii) Load rising linearly from 200 KW to 500 KW in 4 minutes  
iv) Constant load 300 KW for 3 minutes  
v) Regenerative braking for 300 KW to 0 KW in 4 minutes  
vi) Remain idle 3 minutes.  
Sketch the load curve. Determine suitable power rating of a motor. (06 Marks)
- 3 a. Draw necessary circuit diagram and wave forms and explain the operation of a drive using single phase half controlled converter control of separately excited DC motor. (10 Marks)  
b. A 220V, 960 rpm, 12.8A separately excited DC motor has armature circuit resistance of 2 ohms and inductance of 150mH. It is fed from a single phase half controlled rectifier with an AC source voltage of 230V, 50Hz calculate the motor torque for  $\alpha = 60^\circ$  and speed = 600 rpm. (10 Marks)
- 4 a. Explain three phase fully controlled rectifier control of separately excited DC motor state the equations for  $V_a$ ; average output voltage, and  $\omega_m$ ; speed. (08 Marks)  
b. Explain multiquadrant operation of a separately excited DC motor using dual converters. (06 Marks)  
c. A 230V, 960 rpm, 100A separately excited DC motor has an armature circuit resistance of 0.06 ohm and inductance of 150mH. The motor is fed from a chopper having source voltage of 230V, assuming continuous conduction calculate the duty ratio of the chopper for motoring operation at 1.25 times rated torque and 450 rpm. (06 Marks)

**PART – B**

- 5 a. Draw necessary circuit diagram and explain the operation of any two of the following starting methods as used for induction motors.
- Star - delta starting (08 Marks)
  - Korndorfer starter (closed transition auto transformer)
  - Rotor resistance starting. (12 Marks)
- b. A 2200V, 2600Kw, 735 rpm, 50Hz 8 pole, 3 $\phi$  induction motor has following parameters referred to stator,  $R_s = 0.075\Omega$ ,  $R_r = 0.1\Omega$ ,  $X_s = 0.45\Omega$ ,  $X'_r = 0.55\Omega$  stator winding is delta connected and consists of two sections connected in parallel. Calculate the maximum value of line current during starting and i) full load torque ii) starting torque.
- 6 a. Draw the block diagram, and explain the operation of closed loop slip controlled PWM inverter drive. (10 Marks)
- b. Describe and compare static scherbius drive with static Kraner drive (Use sketches). (10 Marks)
- 7 a. Describe how a synchronous motor may be started using its damper windings. (08 Marks)
- b. Draw necessary block diagram and explain variable frequency control of multiple synchronous motors, state one application. (08 Marks)
- c. Compare dynamic braking with regenerative braking using a synchronous motor. (04 Marks)
- 8 a. With necessary diagrams explain the requirements of a rolling mill drive. (07 Marks)
- b. Sketch and describe a paper mill drive. (06 Marks)
- c. Explain any one type of cement mill drive with sketch. (07 Marks)

\* \* \* \* \*