Seventh Semester B.E. Degree Examination, June/July 2015 Industrial Drives and Applications

Time: 3 hrs. Max. Marks: 100

Note: Answer any FIVE full questions, selecting atleast TWO questions from each part.

PART - A

1 a. What are the advantages of electric drive system?

(04 Marks)

- b. Mention the main factors which decide the choice of an electrical drives for a particular application. (06 Marks)
- c. A motor drives two loads. The rotational load coupled to the motor through reduction gear with a = 0.1 and efficiency of 90%. The load has a moment of inertia of 10kg/m^2 and a torque of 10N-m. Other load has a translational motion and consists of 1000kg weight to be lifted up at a uniform speed of 1.5 m/sec. The coupling between this load and motor has an efficiency of 85% motor has an inertia of 0.2kg/m^2 and runs at a constant speed of 1420 rpm. Calculate equivalent inertia and torque refereed to the motor shaft and also power developed by the motor
- 2 a. Derive an expression to determine the power ratings of electric motors for continuous duty for fluctuating and intermittent loads by equivalent current, torque and power methods.

(10 Marks)

- b. Explain the method of determination of motor rating for short time duty loads. (06 Marks)
- c. A constant speed motor has the following duty cycle
 - i) Load rising linearly from 200 to 500kW for 4 minutes.
 - ii) Uniform load of 400kW for 2 minutes.
 - Regenerative power returned to the supply, reducing linearly from 400kW to 0 kW for 3 minutes; and remains idle for 4 minutes. Calculate the power rating of the motor. Assuming loss to be proportional to (power)². (04 Marks)
- a. With circuit diagram and wave forms explain the operation of continuous conduction mode for a single phase half controlled rectifier of separately excited d.c. motor. And also obtain the average output voltage and speed/torque equation. (10 Marks)
 - b. A 220V, 1500 rpm, 10A separately excited d.c. motor is fed from a single phase fully controlled rectifier with an a.c. source voltage of 230V, 50Hz, Ra = 2Ω. Conduction can be assumed to be continuous. Calculate the firing angles for i) Half the rated motor torque and 500rpm; ii) Rated motor torque and -1000 rpm.
- 4 a. With circuit diagram and waveforms explain three phase fully controlled rectifier control of separately excited d.c. motor. (10 Marks)
 - b. A 230V, 1200rpm, 15A separately excited motor has an armature resistance of 1.2Ω. Motor is operated under dynamic braking with chopper control. Braking resistance has a value of 20Ω. Calculate: i) The duty ratio of chopper for motor speed of 1000rpm and braking torque equal to 1.5 times the rated motor torque; ii) Motor speed for duty ratio of 0.5 and motor torque equal to its rated torque.

PART - B

- 5 a. Explain the effect of unbalanced voltages and single phasing on the induction motor performance. (10 Marks)
 - b. A 400V, star connected, 3 phase 6 pole, 50Hz induction motor has following parameters referred to the stator $R_S = R_r^1 = 1\Omega$, $X_S = X_r^1 = 2\Omega$. For regenerative braking operation calculate the maximum overhauling torque and range of speed for safe operation. (10 Marks)
- 6 a. With circuit diagram and wave form, explain the operation of voltage source inverter fed induction motor drives. (10 Marks)
 - b. With circuit diagram and speed/torque curves explain the operation of static Scherbius drive for slip power recovery scheme. (10 Marks)
- 7 a. Explain the operation of synchronous motor from fixed frequency supply. (10 Marks)
 - b. With circuit diagram, explain the self controlled synchronous motor drive employing load commutated thyristor inverter. (10 Marks)
- 8 a. Classify and explain the drives used in cement industry (10 Marks)

b. Explain the various stages in paper mill and motors used in various stages. (10 Marks)