

Seventh Semester B.E. Degree Examination, Dec.2018/Jan. 2019
VLSI Circuits and Design

Time: 3 hrs.

Max. Marks:100

**Note: Answer FIVE full questions, selecting
atleast TWO questions from each part.**

PART – A

- 1 a. With neat diagrams, explain the working of enhancement mode nMOS transistor, for different values of V_{DS} . (08 Marks)
- b. Explain the nMOS fabrication process with neat diagram. (10 Marks)
- c. Compare CMOS and bipolar techniques. (02 Marks)
- 2 a. Discuss the drain to source I_{ds} versus V_{ds} relationship for non saturated and saturated regions. (10 Marks)
- b. Define Z_{pu} Z_{dp} . Show that pull-up to pull-down ratio for nMOS inverter driven through one or more pass transistor is $\frac{Z_{pu2}}{Z_{pd2}} = 8:1$. (10 Marks)
- 3 a. With neat diagrams express the Lambda based design rules as applicable to MOS layers, transistors, and contacts. (10 Marks)
- b. Draw circuit symbol and stick diagram for CMOS inverter. (04 Marks)
- c. Draw the stick diagram and layout for an nMOS two way selector, with enable input. (06 Marks)
- 4 a. What is sheet resistance? Calculate sheet resistance of transistor channel if $L = 8\lambda$, $W = 2\lambda$, if n transistor channel $R_s = 10^4 \Omega/\text{square}$. (06 Marks)
- b. Derive an expression for rise time and fall time of CMOS inverter. (06 Marks)
- c. Write a note on BiCMOS drivers. (08 Marks)

PART – B

- 5 a. Explain different scaling models by considering the relevant diagram of an nMOS transistor. (06 Marks)
- b. Obtain the scaling factors for the following transistor parameters, by considering the constant voltage scaling model:
 - i) Gate area
 - ii) Gate capacitance per unit area
 - iii) Gate capacitance. (06 Marks)
- c. By considering a suitable example, compare the metal inter connect and electro-optical interconnect models. (08 Marks)
- 6 a. Explain the structured design approach for a parity generator circuit and draw the nMOS diagram of the basic cell. (10 Marks)
- b. Explain the structured design of bus arbitration logic for n lines. Also write the circuit diagram and stick diagram for a single cell. (10 Marks)
- 7 a. Explain the basic bus architecture for 4 bit arithmetic process with neat diagrams. (10 Marks)
- b. Explain with neat diagram 4×4 barrel shifter. (10 Marks)
- 8 a. Define explain regularity. (04 Marks)
- b. Explain the design of 4-bit adder with adder element requirements. (08 Marks)
- c. Draw the structure of a multiplexer based adder logic with stored and buffered sum output. (08 Marks)

* * * * *

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
 2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.