

Seventh Semester B.E. Degree Examination, Dec.2014/Jan.2015
VLSI Circuits & Design

Time: 3 hrs.

Max. Marks: 100

Note: 1. Answer FIVE full questions, selecting at least TWO questions from each part.
 2. Missing data suitably assumed.

PART – A

- 1 a. Discuss Moore's law, with graph. (04 Marks)
- b. Compare speed / power performance of available IC technologies. (06 Marks)
- c. Explain in detail the process of Nmos fabrication with neat diagrams. (10 Marks)

- 2 a. Discuss drain-to-source current versus voltage relationships for non-saturated and saturated regions. (10 Marks)
- b. Define Z_{pu} and Z_{pd} . Show that pull-up to pull-down ratio for Nmos inverter driven through one or more pass transistors is $\frac{Z_{pu}}{Z_{pd}} = 8 : 1$ (10 Marks)

- 3 a. Write a note on MOS layers. (04 Marks)
- b. Draw circuit symbols and stick diagrams of, i) NMOS ii) CMOS inverter. (10 Marks)
- c. Draw the stick diagram and layout for an NMOS two way selector, with enable input. (06 Marks)

- 4 a. What is area capacitance and standard unit of capacitance? Calculate the total area capacitance for the multilayered structure shown in Fig. Q4 (a). Assume for $5\mu\text{m}$ technology:
 i) Metal 1 to substrate : $0.075 \times 10^{-4} \text{ pF}/\mu\text{m}^2$.
 ii) Polysilicon to substrate : $0.1 \times 10^{-4} \text{ pF}/\mu\text{m}^2$.
 iii) Gate to channel : $1 \times 10^{-4} \text{ pF}/\mu\text{m}^2$. (10 Marks)

 


Fig. Q4 (a)

- b. Derive an expression for rise time and fall time of CMOS inverter. (06 Marks)
- c. What is sheet resistance? Calculate sheet resistance of transistor channel if $L = 8\lambda$, $W = 2\lambda$, if n-transistor channel $R_s = 10^4 \Omega/\text{square}$. (04 Marks)

PART - B

- 5 a. What are the different scaling models and scaling factors? Draw scaled nMOS transistor diagram. (08 Marks)
- b. Indicate scaling factors for,
i) Gate area ii) Gate capacitance
v) Power speed product vi) Channel resistance. (06 Marks)
c. Write a note on limitations of scaling. (04 Marks)
- 6 a. Explain in detail: i) Pseudo-nMOS logic and ii) Dynamic cMOS logic. (10 Marks)
- b. Explain the structured design of bus arbitration logic for n lines. Also, write the circuit diagram and the stick diagram for a single cell. (10 Marks)
- 7 a. Explain the general arrangement of a 4-bit arithmetic processor. (10 Marks)
- b. Explain the operation of 4×4 cross bar switch with a neat diagram. (10 Marks)
- 8 a. Explain the some observations on the design process. (06 Marks)
- b. What is regularity? Explain. (04 Marks)
- c. With a neat diagram and relevant expressions, explain the implementation of a 4 bit Alu, using full adders. (10 Marks)
