

USN

--	--	--	--	--	--	--	--	--	--

10EE764

Seventh Semester B.E. Degree Examination, June/July 2018
VLSI Circuits and Design

Time: 3 hrs.

Max. Marks: 100

**Note: Answer FIVE full questions, selecting
at least TWO questions from each part.**

PART - A

- 1 a. Explain in detail, the process of n-MOS fabrication with the help of necessary fabrication structures. (10 Marks)
 b. Discuss Moore's law. Explain the working of enhancement mode of transistor with different values of V_{ds} . (10 Marks)
- 2 a. Derive an expression for I_{ds} for both saturated as well as non saturated region. (10 Marks)
 b. Define Z_{pu}/Z_{pd} . Show that pull up to pull down ratio for nMOS inverter driven through one or more pass transistor is 8 : 1. (10 Marks)
- 3 a. Draw the monochrome stick diagram of n-MOS shift register cell. (06 Marks)
 b. Define stick diagram. Explain the encoding used for simple n-MOS process. (06 Marks)
 c. What are the advantages of complementary transistor pull-up for an inverter? With relevant diagram, explain the CMOS inverter operation in different region. (08 Marks)
- 4 a. Define sheet resistance, square capacitance and delay unit, explain it same for different technologies. (06 Marks)
 b. Estimate CMOS inverter delay in terms of rise time and fall time. (06 Marks)
 c. Calculate the total capacitance in picofarads between the substrate and structure as shown in Fig. Q4 (c) for $\Lambda = 5 \mu m$. Use standard values. (08 Marks)

 


Fig. Q4 (c)

PART - B

- 5 a. Derive the scaling factors for the following device parameter by considering constant electric field scaling model:
 - (i) Gate capacitance
 - (ii) Maximum operating frequency
 - (iii) Current density.
 - (iv) Channel resistance.
 - (v) Power dissipation per gate P_g . (10 Marks)
- b. Discuss in detail the limitation of scaling and limits due to subthreshold currents. (10 Marks)

10EE764

- 6 a. Write the structure and stick diagram of nMOS, CMOS 2 I/P nand gates. (06 Marks)
b. Prove that for pseudo nMOS logic $Z_{pu} / Z_{pd} = \frac{3}{1}$. (06 Marks)
c. Write note on:
(i) General logic function block.
(ii) Multiplexer. (08 Marks)
- 7 a. Explain the design of 4-bit shifter. (10 Marks)
b. Define regularity. Explain the design of an ALU subsystem. (10 Marks)
- 8 Write short notes on:
a. Some general consideration in subsystem design processes.
b. Dynamic shift register.
c. Dynamic CMOS logic.
d. Gray code to binary code converter. (20 Marks)

* * * * *