

USN

--	--	--	--	--	--	--	--	--	--

<b>NEW SCHEME</b>
-------------------

**Eighth Semester B.E. Degree Examination, Dec.06 / Jan.07**  
**Electrical and Electronics Engineering**  
**HVDC transmission**

Time: 3 hrs.]

[Max. Marks:100

**Note: I. Answer any FIVE full questions.**

- 1
  - a. List the advantages and disadvantages of HVDC transmission. (08 Marks)
  - b. Mention the applications of DC transmission. (06 Marks)
  - c. Explain the recent trends in HVDC transmission. (06 Marks)
  
- 2
  - a. Explain the simplified analysis of Graetz circuit without overlap. (03 Marks)
  - b. Derive an expression, in the above circuit, for the D.C. voltage, and the rms value of the fundamental component of AC line current. Also show  $\cos \phi = \cos \alpha$ . (09 Marks)
  - c. A Graetz circuit is fed by a transformer and the pertaining data are :  
 Output voltage per phase of transformer = 100 kV (rms) ;  
 Reactance per phase of transformer = 5% ;  
 Transformer power rating = 100 MVA ;  
 Firing angle  $\alpha = 30^\circ$ ,  
 Overlap angle  $u = 30^\circ$ ,  
 Calculate load current, terminal voltage on D.C. side. (08 Marks)
  
- 3
  - a. Discuss the merits and demerits of constant current versus constant voltage control of power in a HVDC system. (05 Marks)
  - b. State the desired features of control for HVDC system. (05 Marks)
  - c. A bipolar HVDC link rated at  $\pm 500$  kV, 500 MW is delivering 400 MW, at the inverter end. The AC voltage at the inverter end is 400 kV having commutating resistance of  $2\Omega$  and DC voltage of  $\pm 475$  kV. Calculate
    - i) Excitation angle of inverter.
    - ii) Voltage at rectifier.
    - iii) Length of DC line.
    - iv) Power at rectifier.
 Given loss in DC line is 12 MW and resistance is  $10\text{ m}\Omega$  per km. (10 Marks)
  
- 4
  - a. What are the various kinds of DC links? Draw the figures and briefly explain. (05 Marks)
  - b. Explain the basic principle of DC link control with the help of equivalent circuit for 2 terminal DC link in steady state. (05 Marks)
  - c. Draw the combined characteristic of rectifier and inverter and briefly explain. (05 Marks)
  - d. Explain constant current characteristic with the help of schematic diagram. (05 Marks)
  
- 5
  - a. Mention the different types of faults that can occur in converters. (02 Marks)
  - b. Describe commutation failure and its effects. (06 Marks)

Contd...2

- 5 c. What are the basic principles of over current protection in D.C. systems? Draw the schematic diagram for over current protection in a pole. (06 Marks)
- d. Explain the causes of over voltages in a converter station. (06 Marks)
- 6 a. List the functions of smoothing reactor. (05 Marks)
- b. Find the inductance of the DC reactor required to prevent consequent commutation failure in the inverter described below.  
Number of bridges per pole = 2  
Rated voltage per bridge = 200 kV  
Rated current = 1.8 kA  
 $I_{S2} = 10 \text{ kA}$   
Frequency = 60 Hz. (06 Marks)
- c. What are the major problems in the current interruption in DC circuits? (04 Marks)
- d. List the problems associated with the injection of harmonics from HVDC converters into AC system and D.C. line. (05 Marks)
- 7 a. Define the following relating to criteria of design of harmonic filters.  
i) Harmonic distortion.  
ii) Telephone influence factor.  
iii) Telephone harmonic form factor. (09 Marks)
- b. List the various types of AC filters used. (03 Marks)
- c. Draw the circuit diagram and impedance characteristics as a function of the frequency of the above filters. (06 Marks)
- d. What is the main difference in the design criteria of AC and DC filters? (02 Marks)
- 8 a. What are the requirements of a good simulation tool? (04 Marks)
- b. List some of the problems that can be studied using a DC simulator. (04 Marks)
- c. What are the main advantages and disadvantages of digital simulation? (06 Marks)
- d. Explain briefly the three different ways of modeling a valve / converter for digital dynamic simulation. (06 Marks)

\*\*\*\*\*

