

--	--	--	--	--	--	--	--	--	--

Eighth Semester B.E. Degree Examination, Dec.09/Jan.10
HVDC Transmission

Time: 3 hrs.

Max. Marks:100

Note: Answer any FIVE full questions.

1.
 - a. Compare the ac and dc transmission systems based on their technical performance. (08 Marks)
 - b. What are the different configurations for dc interconnection? Which is the most economic configuration? (06 Marks)
 - c. Explain the criteria to select the voltage level for long distance bulk power transmission. (06 Marks)

2.
 - a. Define valve utilisation factor and transformer utilization factor. Calculate these values when $q = 3$, $r = 1$ and $s = 2$. (08 Marks)
 - b. Show that the reactive power consumed by the converter increases with the increase in the firing angle. (06 Marks)
 - c. Draw the dc voltage waveforms of the Graetz circuit for firing angles $\alpha = 0, 30^\circ, 60^\circ, 90^\circ, 120^\circ, 150^\circ$ and 180° . (06 Marks)

3.
 - a. Explain the principle of dc link control with the help of equivalent circuit for two terminal dc link. (10 Marks)
 - b. List the derived features of HVDC link control. (04 Marks)
 - c. What is current margin? Why is current controller required at both rectifier and inverter stations. (06 Marks)

4.
 - a. With usual notations show that the current on AC side of 12 pulse converter is given by

$$i_A = \frac{4\sqrt{3}I_d}{\pi} \left[\cos \omega t - \frac{1}{11} \cos 11\omega t + \frac{1}{13} \cos 13\omega t - \dots \right].$$
 (12 Marks)
 - b. Define the different performance indices used to measure the telephone interference in case of filters. (08 Marks)

5.
 - a. What is commutation failure? What are the effects of single commutation failure? (06 Marks)
 - b. Describe the causes of over voltages in a converter station. (09 Marks)
 - c. Draw the schematic diagram of the over voltage protection of converter station. (05 Marks)

6.
 - a. List the main functions of smoothing reactor. (06 Marks)
 - b. What are the three basic types of faults in converters? (06 Marks)
 - c. Explain the basic concept of DC circuit interruption. (08 Marks)

7.
 - a. What are the various tools available for the simulation of dynamic system? (04 Marks)
 - b. Explain dynamic digital simulation of HVDC systems. Bring out its merits and demerits. (08 Marks)
 - c. Explain the HVDC converter model for dynamic analysis. (08 Marks)

8. Write short notes on :
 - a. Modern trends in dc transmission
 - b. Power control in HVDC transmission systems
 - c. Non characteristic harmonics
 - d. HVDC simulator (physical model). (20 Marks)
