

--	--	--	--	--	--	--	--	--	--

NEW SCHEME


Eighth Semester B.E. Degree Examination, May 2007
Electrical and Electronics Engineering
HVDC Transmission

Time: 3 hrs.]

[Max. Marks:100

Note : Answer any FIVE full questions.

- 1 a. Compare AC and DC transmission systems briefly. (08 Marks)
- b. Explain the factors to be considered while planning for HVDC transmission. (06 Marks)
- c. Explain the recent trends in HVDC transmission. (06 Marks)
- 2 a. Derive an expression for terminal voltage of the converter considering firing delay and communication overlap. (10 Marks)
- b. A bridge connected rectifier is fed from 220 kV/110 kV transformer with primary connected to 220 kV
 - i) Determine the dc output voltage when the commutation angle is 15° and the delay angle is 0° (zero degree). (06 Marks)
 - ii) If the rectifier delivers 800 amps, determine the effective reactance / phase for $\alpha = 30^\circ$, E_{d1} (line secondary voltage of the rectifier transformer) = 94, 115 kV and dc voltage, $V_d = 100$ kV. (06 Marks)
- c. Name 4 (tons) applications of DC transmission. (04 Marks)
- 3 a. Draw the ideal and actual control characteristics of rectifier and inverter and explain briefly. (10 Marks)
- b. Explain stability of control by considering damping circuit. (10 Marks)
- 4 a. Explain any three types of converter faults. (12 Marks)
- b. Explain the causes of over voltages in a converter stations. (08 Marks)
- 5 a. What are the basic principles of over voltage protection and over current protection in HVDC system? (10 Marks)
- b. Write 6 functions of smoothing reactor. (06 Marks)
- c. A circuit breaker is used to interrupt a DC line. The parameters are as follows:
DC current of 50 A, system voltage = 250 V, breaker counter voltage = 500 V and DC line inductance is 1 Henry. Calculate the energy absorbed by the breaker. (04 Marks)
- 6 a. Explain briefly the function and basic concepts of DC circuit breaker. (10 Marks)
- b. What are the different types of AC filter? Explain briefly with relevant figures.(10 Marks)
- 7 a. Differentiate characteristic and non-characteristic harmonics. (08 Marks)
- b. For a converter unit shown in fig.7(b) below, neglecting overlap, find expression for i_{A1} , i_{A2} and i_{A} . (06 Marks)

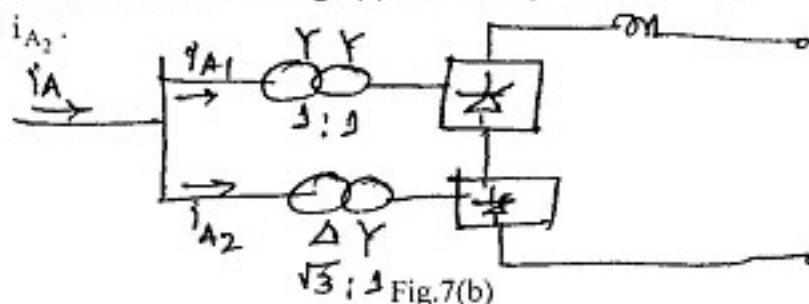

- c. What are the applications of DC simulators? (06 Marks)
- 8 a. Explain: i) Valve and converter model ii) Controller model. (10 Marks)
- b. Explain any two:

i) Constant current control	ii) Surge arrestors
iii) HVDC link operation	iv) Parity simulator.