

--	--	--	--	--

Eighth Semester B.E. Degree Examination, May/June 2010
HVDC Transmission

Time: 3 hrs.

Max. Marks:100

**Note: Answer any FIVE full questions, selecting
at least TWO questions from each part.**

PART – A

- 1 a. Describe advantages and disadvantages of HVAC and HVDC power transmission systems for transmitting large bulks of power. (10 Marks)
- b. Mention the applications and limitations of HVDC power transmission. (06 Marks)
- c. With a neat sketch, explain merits and demerits of homopolar link. (04 Marks)

- 2 a. With the help of a single line diagram, explain the role of each component in a typical converter station. (10 Marks)
- b. Derive an expression for
 - i) Value utilization for
 - ii) Transformer utilization factor for a six pulse Greatz circuit. (10 Marks)

- 3 a. Analyze the Greatz circuit without overlap and prove that $\cos\phi = \cos\alpha$, where $\cos\phi$ is input supply power factor and α is the firing angle delay, with assumptions made. (12 Marks)
- b. A bridge converter is supplied by an input transformer and the details are as follows.

Output voltage per phase of transformer	= 200 kV (rms)
Reactance per phase of transformer	= 5%
Transformer power rating	= 100 MVA
Firing angle α	= 30°
Overlap angle μ	= 15°

 Calculate the load current and terminal voltage on DC side. (08 Marks)

- 4 a. Discuss the merits and demerits of constant current versus constant voltage control of power in a HVDC system. (06 Marks)
- b. List the desired features of HVDC link control. (06 Marks)
- c. Write a note on constant minimum ignition angle control of HVDC system. (08 Marks)

PART – B

- 5 a. Enumerate the functions of smoothing reactor in case of HVDC transmission systems. (06 Marks)
- b. Calculate the value of smoothing reactor for a HVDC system of rated voltage 100 kV and rated current 1250 KA. Assume S_i factor as 0.8. (04 Marks)
- c. Explain stability of control by considering a damping circuit. (10 Marks)

- 6 a. With reference to HVDC converter control system bring out the limitations of manual control. (05 Marks)
- b. What is the role of a power controller in a HVDC converter? Explain. (05 Marks)
- c. Describe with the aid of V.I characteristics the meaning of 'mode ambiguity' and how it can be stabilized. (10 Marks)
- 7 a. Give the procedure of detecting line faults so as to ensure DC line protection. (08 Marks)
- b. With the aid of a block diagram, explain Constant Extinction Angle (CEA) control of HVDC converter. (07 Marks)
- c. Explain how current oscillations are minimized using anode dampers. (05 Marks)
- 8 Write explanatory notes on :
- a. Starting and stopping of DC links
- b. Current margin and its significance
- c. Thyristor valve design
- d. Choice of best circuit for HVDC converters. (20 Marks)

* * * * *