

Eighth Semester B.E. Degree Examination, Dec 08 / Jan 09
VLSI Circuits and Design

Time: 3 hrs.

Max. Marks:100

Note : Answer any FIVE full questions.

- a. With the help of cross sectional view and typical processing steps, explain the n - well CMOS fabrication process. (12 Marks)
- b. Briefly discuss the comparison between the CMOS and Bipolar technologies. (08 Marks)
- a. Discuss the aspects of MOS Transistor threshold voltage with relevant equation. (06 Marks)
- b. An inverter (nMOS) is driven directly by another inverter. Show that $\frac{Z_{pu}}{Z_{pd}} = \frac{4}{1}$. (06 Marks)
- c. With a neat diagram, explain the Latch-up in CMOS circuits. (08 Marks)
- 3 a. With neat diagram, explain the design rules for wires, transistor design rules and contacts. (10 Marks)
- b. Draw the stick diagram of inverter with respect to i) nMOS ii) CMOS iii) BiCMOS. (10 Marks)
- a. For the circuit shown in figure 4(a), show that the transit time τ_{sd} and the delay time τ are interchangeable. (08 Marks)

 


Fig.4(a)

- b. Explain the working of a inverting type nMOS super buffer. (06 Marks)
- c. In brief, explain the various components which contribute to the overall wiring capacitance. (06 Marks)
- a. Calculate the effects of scaling on the following parameters. (10 Marks)
 - i) Gate delay T_d .
 - ii) Channel resistance R_{CN} .
 - iii) Current density J .
 - iv) Switching energy per gate E_g .
 - v) Power - speed product P_T .
- b. Compare the propagation delay of metal interconnect and optical interconnect by calculating the numerical value in both interconnects. (10 Marks)
- 6 a. Obtain the MOS diagram and slide diagram of a 2 input NOR gate with respect to i) nMOS ii) CMOS. (07 Marks)
- b. Explain the structural design of parity generator and hence derive one - bit basic cell. (07 Marks)
- c. Draw the logic arrangement of 4-line gray code to binary code converter and obtain one possible arrangement for an exclusive OR - gate. (06 Marks)
- 7 a. Design a 4 - bit shifter using i) cross bar switch ii) Barrel - type. (10 Marks)
- b. Explain the design process of 4 - bit adder and obtain the multiplexer based adder logic arrangement. (10 Marks)
- 8 Write short notes on:

a. Alternate forms of pullup	c. Scaling models.
b. MOS design styles	d. Switch logic.

 (20 Marks)
