

M.Tech. Degree Examination, May/June 2010
Digital System Design using VHDL

Time: 3 hrs.

Max. Marks:100

Note: Answer any FIVE full questions.

- 1
 - a. Explain entity and data flow modeling, with examples. (06 Marks)
 - b. Write a behavioral description of JK flip-flop with active low clock, set and reset using process statement. (06 Marks)
 - c. Write a structural description of 4-bit adder. (08 Marks)

- 2
 - a. Explain the following with examples: i) Loop statement ii) Case statement
 iii) Assert statement iv) Wait statement (12 Marks)
 - b. Write a VHDL model for the 74194 4-bit bidirectional shift register, with following functions. The CLR_b input is asynchronous and active low and overrides all the other control inputs. If the control inputs S₁ = S₀ = 1, the register is loaded in parallel. If S₁=1 and S₀=0, the register is shifted right and SDR (Serial Data Right) is shifted into Q₃. If S₁=0 and S₀=1, the register is shifted left and SDL is shifted into Q₀. If S₁=S₀=0, no action occurs. (08 Marks)

 


Fig. Q2 (b)

- 3
 - a. Bring out the differences between a VHDL function and a VHDL procedure. (05 Marks)
 - b. Write a VHDL function that adds two 4-bit vectors and a carry and it returns a 5 bit sum. (05 Marks)
 - c. List the data types in VHDL. Explain any three types with example, showing type declaration and object declaration of that type. (10 Marks)

- 4
 - a. Draw the block diagram, state graph and VHDL program for the behavioral model of a 4×4 multiplier. (12 Marks)
 - b. Write a VHDL description for a divider that divides a 8-bit dividend by a 3-bit divisor to give a 5-bit quotient. (08 Marks)

- 5
 - a. Give an execution graph and develop a micro VHDL description of a system that performs the following computation without using a two-operand adder.
 Inputs : $x, y \in \{-128, \dots, 127\}$
 Output: $z \in \{-256, \dots, 508\}$
 Function : $z = \begin{cases} \frac{4[(x+|y|)]}{2} & \text{if } x < |y| \\ 4x & \text{otherwise} \end{cases}$ (10 Marks)
 - b. Classify the control of the system according to its structure and explain. (05 Marks)
 - c. What are the characteristics of the implementation of an RTL system at the binary level? (05 Marks)

- 6 a. Outline the procedure for designing RTL systems with necessary generalized VHDL descriptions for data subsystem and control subsystem. (10 Marks)
- b. Explain structure of a micro programmed controller, with block a diagram. (10 Marks)
- 7 a. Draw the general structure of a data sub system, suitable for RTL sequence of a micro programmed system and explain the functions of the various modules. (10 Marks)
- b. Write the VHDL behavioral description of the above data subsystem. (10 Marks)
- 8 a. Draw the flowchart and SM chart for floating point multiplication. (10 Marks)
- b. Draw the internal organization and timing diagram for a memory subsystem suitable for a typical microcomputer. (05 Marks)
- c. Write a VHDL description using case statement for 2-to-4 decoder. (05 Marks)