

--	--	--	--	--	--	--	--	--	--

**M.Tech. Degree Examination, December 2011**  
**CMOS VLSI Design**

Time: 3 hrs.

Max. Marks:100

**Note: 1. Answer any FIVE full questions.**  
**2. Assume suitable missing data, if any.**  
**3. Draw neat diagrams, wherever necessary.**

- 1 a. With a neat diagram, explain the behaviour of nMOS enhancement mode MOSFET in different regions and draw the VI characteristics. (10 Marks)
- b. Explain the following : (10 Marks)
  - i) Channel length modulation.
  - ii) Threshold voltage – body effect.
- 2 a. For a CMOS inverter, calculate the shift in the transfer characteristic when  $\beta_n/\beta_p$  ratios are 0.1, 1, 5 and draw the transfer characteristic with  $\beta$  ratio (use typical values). (08 Marks)
- b. Explain the working of a BiCMOS inverter using MOS transistors and resistors and draw the input output characteristics. (06 Marks)
- c. Explain the operation of a Pseudo – nMOS inverter and draw DC transfer characteristics. (06 Marks)
- 3 a. Using  $\lambda$  - based design rules, draw the layout for a nMOS 3 input NOR gate, using the following transistor  $L/w$  ratios. (12 Marks)
  - i) p.u. transistor = 8:1
  - ii) p.d. transistors = 1:2, 1:2, 1:2.
 Place the output point on the polysilicon layer.
- b. Calculate CMOS inverter pair delays in terms of  $T$ , for the following diagram : (08 Marks)



Fig.Q.3(b)

- 4 a. Draw the schematic and layout for given CMOS logic function  $A = \overline{X.Y + W.Z}$ . (06 Marks)
- b. Design and implement 2:1 MUX based 8:1 MUX using transmission gates. (08 Marks)
- c. Using the minimum number of transistors, draw the schematic diagram for a given CMOS logic function  $Z = \overline{ABC + BCD + BE}$ . (06 Marks)
- 5 a. An off chip capacitance load of 5pf is to be driven from nMOS inverters. Set out suitable arrangements giving appropriate channel  $L/w$  ratios. Calculate the number of inverter stages required, the width factor, input capacitance of each inverter and delay exhibited by the overall arrangement. Use the  $5\mu\text{m}$  technology. (10 Marks)

- b. Determine the node voltages  $V_1$ ,  $V_2$ ,  $V_3$ ,  $V_4$  and  $V_5$  for the following pass transistor diagram where  $V_{DD} = 5V$  and  $V_{in} = 1.5V$ . (05 Marks)

 


Fig.Q.5(b)

- c. Derive the scaling factors of the following MOS parameters : (05 Marks)
- Gate delay –  $T_d$  ;
  - Gate capacitance –  $C_g$ .
- 6 a. What is voltage bootstrapping? Explain the dynamic techniques, using transmission gates and dynamic CMOS logic. (10 Marks)
- b. Explain the operation of clocked NOR based SR latch and JK latch. (10 Marks)
- 7 a. What is latch up? Explain the effect of latch up in p – well CMOS inverter structure. (10 Marks)
- b. Explain the operation of domino CMOS structure. (05 Marks)
- c. Analyze a nMOS current mirror circuit. (05 Marks)
- 8 a. Explain accumulation, depletion and channel inversion in an enhancement mode nMOS transistor. (08 Marks)
- b. What is scaling? List the advantages of scaling. (04 Marks)
- c. Explain the operation of a differential amplifier. (08 Marks)

\* \* \* \* \*