

--	--	--	--	--	--	--	--	--	--


M.Tech. Degree Examination, December 2011
Digital Circuits and Logic Design

Time: 3 hrs.


Max. Marks:100

Note: Answer any FIVE full questions.

- 1 a. Explain the concept of threshold logic. (06 Marks)
- b. Discuss the following : (06 Marks)
 - i) Elementary properties ;
 - ii) Unite function.
- c. Show that a threshold logic realization of a full – adder requires only two threshold elements. (Note : both sum and carryout must be generated). (08 Marks)
- 2 a. Explain the static hazard and hazard free-circuits, with example. (08 Marks)
- b. What are critical and sub-critical errors? Determine the same for AND, OR, NAND, NOR and XOR gates. (06 Marks)
- c. Explain the basic structure of a quadded network with the help of diagram. (06 Marks)
- 3 a. Explain restoring-organs. (04 Marks)
- b. Apply Boolean difference method to test wire ‘h’ in the circuit shown in Fig.Q.3(b). (06 Marks)

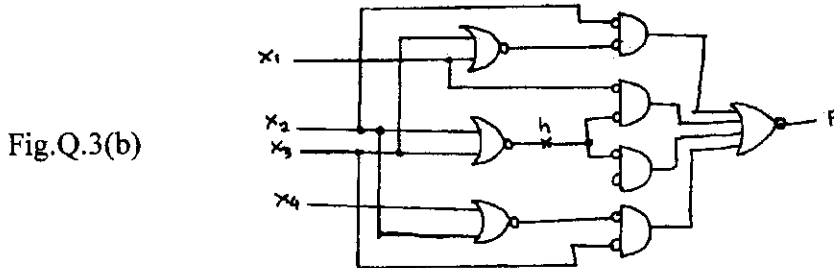

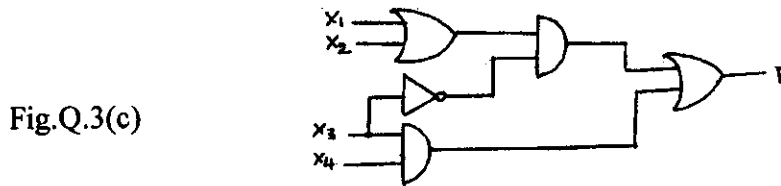- c. For the circuit shown in Fig.Q.3(c), find all tests to detect the faults x_3 , s-a-0 and s-a-1. (10 Marks)



- 4 a. Write a note on fault-detection by path sensitizing. (07 Marks)
- b. Explain the systematic generation of minimal fault-detection by generating b-tests.(07 Marks)
- c. List the capacities and limitations of finite state machines. (06 Marks)
- 5 a. What are compatible states? For the tabular column Table Q.5(a) shown machine ‘M’. Find the augmented machine and corresponding minimal machines. (10 Marks)

PS	NS, Z	
	x = 0	x = 1
A	A, 0	C, 0
B	B, 0	B, -
C	B, 0	A, 1

Table Q.5(a)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

- b. What is merger graph? Draw the merger graph for the incompletely specified machine M shown in Table Q.5(b). (10 Marks)

PS	NS, Z			
	I ₁	I ₂	I ₃	I ₄
A	-	C, 1	E, 1	B, 1
B	E, 0	-	-	-
C	F, 0	F, 1	-	-
D	-	-	B, 1	-
E	-	F, 0	A, 0	D, 1
F	C, 0	-	B, 0	C, 1

Table Q.5(a)

- 6 a. Prove the following theorems :
- The equivalence partition is unique.
 - If two states S_i and S_j of machine 'M' are distinguishable, then they are distinguishable by a sequence of length n-1 or less, where n is the number of states in 'M'. (08 Marks)
- b. What is a tree? Explain the types of tree. (06 Marks)
- c. Draw the homing tree of m/c 'M' shown in table Q.6(c) and explain it. Write the response of m/c 'M' to the homing sequence 010. (06 Marks)

PS	NS, Z	
	x = 0	x = 1
A	B, 0	D, 0
B	A, 0	B, 0
C	D, 1	A, 0
D	D, 1	C, 0

Table Q.6(c)

- 7 a. What is a diagnosable sequence m/c? Construct testing table and graph for m/c shown in Table Q.7(a). (10 Marks)

PS	NS, Z	
	x = 0	x = 1
A	B, 0	D, 0
B	A, 0	B, 0
C	D, 1	A, 0
D	D, 1	C, 0

Table Q.7(a)

- b. Identify the m/c which is known to have two states and its response to the I/P response X is the o/p sequence Z, as shown below :

Time :	t ₁ -t ₂	t ₂ -t ₃	t ₃ -t ₄	t ₄ -t ₅	t ₅ -t ₆	t ₆ -t ₇	t ₇ -t ₈
x :	1	1	1	0	1	0	1
z :	0	1	0	0	1	0	0

(10 Marks)

- 8 a. What is an experiment? Explain the types of experiments. (05 Marks)
- b. Prove the theorem :
If an n-state machine has a synchronizing, or sequences, then it has one such sequence whose length is at most $\frac{n(n+1)(n-1)}{6}$. (10 Marks)
- c. Write a short note on synchronizing experiments. (05 Marks)
