

--	--	--	--	--	--	--	--	--	--

**M.Tech. Degree Examination, June/July 2015**  
**CMOS RF Circuit Design**

Time: 3 hrs.

Max. Marks: 100

**Note: Answer any FIVE full questions.**

- 1
  - a. Explain the effect of nonlinearity in a typical RF system with respect to gain compression, cross modulation and intermodulation. (12 Marks)
  - b. An amplifier designed to operate at 2GHz with a gain of 10dB has two signals of equal power applied at the input. One is at a frequency of 2GHz and another at a frequency of 2.01GHz. At the output, four tones are observed at 1.99, 2.0, 2.01 and 2.02GHz. The power levels of the tones are -70, -20, -20 and -70 dBm respectively. Determine the  $1IP_3$  and 1dB compression point for this amplifier. (08 Marks)
- 2
  - a. Discuss the different types of noise associated with a MOSFET. Give expressions for each type of noise. (06 Marks)
  - b. Calculate the total output noise power of the following circuit. Neglect channel length modulation. [Express the noise power in terms of current]. (04 Marks)

 


Fig.Q.2(b)

- c. Explain sensitivity and dynamic range with respect to a RF receiver. Derive the expression for spurious free dynamic range (SFDR)? (10 Marks)
- 3
  - a. Compare TDMA, FDMA and CDMA techniques in detail. (06 Marks)
  - b. Explain the architecture of a dual IF heterodyne receiver with a neat block diagram. (08 Marks)
  - c. Discuss the trade off between image rejection and channel selection in a heterodyne receiver. (06 Marks)
- 4
  - a. Explain the Hastley architecture of image reject receiver. Derive the mathematical relation to show that image rejection is possible. (12 Marks)
  - b. Draw a neat sketch of a direct conversion receiver and list the different issues associated with this receiver. (08 Marks)
- 5
  - a. Draw the complete small signal equivalent circuit of MOSFET at high frequency. (05 Marks)
  - b. Explain one method used to generate quadrature signals in an RF receiver. (05 Marks)
  - c. Calculate the unity gain frequency for the n channel MOSFET. (05 Marks)

Given  $C_{gs} = 25\text{fF}$ ,  $C_{gd} = 2\text{fF}$ ,  $I_D = 100\mu\text{A}$  and  $\mu C_{ox} \frac{W}{L} = 160\mu\text{A}/\text{V}^2$ .

  - d. Draw the large signal Eber Moll model for BJT. (05 Marks)

- 6 a. Draw the circuit diagram of a CMOS LNA and explain its operation. (06 Marks)  
b. Define return loss factor of an LNA. Determine the stability condition of a cascade stage which exhibits a high reverse isolation i.e.  $S_{12} \cong 0$  and  $S_{22} \cong 1$ . (04 Marks)  
c. Explain the working of a voltage controlled oscillator with a neat circuit diagram. (06 Marks)  
d. Suggest one method to employ tuning in VCOs. (04 Marks)
- 7 a. Draw the circuit diagram of a double balanced active mixer and explain the principle of operation. (08 Marks)  
b. Differentiate SSB and DSB noise figure with respect to RF receivers and state a relationship among them. (06 Marks)  
c. Explain Hartley oscillator with grounded drain configuration of single transistor oscillator. (06 Marks)
- 8 a. Explain the operation of a charge pump PLL with a neat block diagram. (10 Marks)  
b. Classify power amplifier based on operating point and sketch circuit diagram for class A power amplifier. (05 Marks)  
c. Explain feed forward linearization technique employed in power amplifiers with a conceptual diagram. (05 Marks)

\*\*\*\*\*