

USN

--	--	--	--	--	--	--	--	--	--

14EVE254

Second Semester M.Tech. Degree Examination, June/July 2015
CMOS RF Circuit Design

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions.

1.
 - a. What is inter symbol interference? Explain its effect and methods for reducing. (06 Marks)
 - b. With a neat block diagram explain generic digital transceiver RF system. (06 Marks)
 - c. Explain intermodulation and hence obtain an expression for AIP_3 and relation between 1dB compression point and input IP_3 . (08 Marks)
2.
 - a. Show the phase transitions in QPSK and OQPSK waveforms. (04 Marks)
 - b. With neat diagram explain working of DPSK. Give an example. (08 Marks)
 - c. What is code division multiple access? Explain direct sequence CDMA technique. (08 Marks)
3.
 - a. With a neat block diagram explain, Direct conversion and two step transmitter. (10 Marks)
 - b. Write a block diagram of Hartley image reject receiver architecture and derive an expression for image rejection ratio. (10 Marks)
4.
 - a. Obtain a high frequency small signal equivalent circuit of BJT and explain it (10 Marks)
 - b. Explain the behavior of MOS transistor at very high frequency. (10 Marks)
5.
 - a. Derive an expression for the voltage conversion gain and power gain in bipolar mixers. (10 Marks)
 - b. Write a note on CMOS LNAs. (10 Marks)
6.
 - a. Define phase noise. Explain the effect of phase-noise in RF communication. (08 Marks)
 - b. Explain Noise-power tradeoff in oscillators. (06 Marks)
 - c. Draw the linear model of a phase locked loop (PLL) and derive an expression for closed loop transfer function $H(s)$. (06 Marks)
7.
 - a. What is RF synthesizer? Explain fractional – N synthesizer with an example. (10 Marks)
 - b. Explain the feed forward and feedback linearization technique with its advantages and disadvantages. (10 Marks)
8.
 - a. Write a short note on:
 - (i) Sensitivity of an RF receiver and Dynamic Range.
 - (ii) Sub sampling receiver. (12 Marks)
 - b. Define the following :
 - (i) 1 – dB compression point
 - (ii) Cross modulation
 - (iii) Desensitization
 - (iv) Q of an oscillator. (08 Marks)

* * * * *

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
 2. Any revealing of identification, appeal to evaluator and/or equations written e.g. 42+8 = 50, will be treated as malpractice.