

Second Semester M.Tech. Degree Examination, June/July 2016
Synthesis and Optimization of Digital Circuits

Time: 3 hrs.

Max. Marks:100

Note: Answer any FIVE full questions.

- 1 a. Explain the different microelectronic design styles. (08 Marks)
- b. Explain surjective, injective and bijective functions. (06 Marks)
- c. Define (i) Polar dag (ii) Acyclic graph (iii) Cutset (iv) Complete graph (v) Indegree & Outdegree. (06 Marks)
- 2 a. Find the shortest path for the graph shown in Fig. Q2 (a) using Bellman-Ford algorithm. (10 Marks)

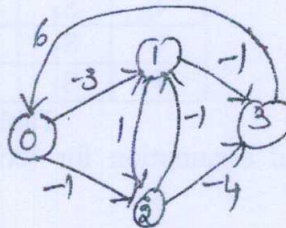


Fig. Q2 (a)

- b. For the function, $f = ab + bc + ac$, compute the expansion on the orthonormal basis. Given that $\phi_1 = a$, $\phi_2 = a'b$ and $\phi_3 = a'b'$. Consider the lower bound of f_{ϕ_i} in each case. (10 Marks)
- 3 a. Consider the following equations:

$$x_1 = x + dx;$$

$$U_1 = [U - (3 * x * u * dx) - (3 * y * dx)];$$

$$y_1 = (y + u * dx);$$

$$c = x_1 < a;$$

$$x = x_1; u = u_1, y = y_1$$
 Implement in VHDL using behavior style. The input and output port signals are of integer and the range is from 0 to 255. (10 Marks)
- b. Explain tree height reduction, constant propagation, dead code elimination, operator strength reduction and loop expansion. (10 Marks)
- 4 a. For the function $f(a,b,c) = a'c' + a'b + bc + ac$ and $f_2(a,b,c) = bc$, obtain the cover of the function, minimum cover and irredundant cover. Represent the same in Boolean cube. (10 Marks)
- b. Represent the function, $f = ab + ac + ab'c' + a'$ in positional cube rotation and check the function is tautology or not. (10 Marks)
- 5 a. Find the expanded cover of the function $f = a'b'c' + ab'c' + a'bc' + a'b'c$ with abc' as a don't care condition. (08 Marks)
- b. Draw the logic network after elimination and decomposition described with primary input variables $\{a, b, c, d, e\}$ and primary output variables $\{w, x, y, z\}$ by the combinational equations:

$$p = ce + de; q = a + b; r = p + a'; s = r + b'; t = ac + ad + bc + bd + e; u = q'c + qc' + qc,$$

$$v = a'd + bd + c'd + ae', w = v, x = s, y = t, z = u.$$
 (12 Marks)

- 6 a. Find the kernel set of $f = ace + bce + de + g$. Also find its co-kernel. (10 Marks)
- b. For the expression, $f = ace + bce + de + g$, write the corresponding matrix representation. Also find the rectangles and its co-rectangles. (10 Marks)
- 7 a. Explain the state encoding for two level circuits using the state table given in table Q7 (a). (10 Marks)

Input	State	Next state	Output
0	S ₁	S ₃	0
1	S ₁	S ₃	0
0	S ₂	S ₃	0
1	S ₂	S ₁	1
0	S ₃	S ₅	0
1	S ₃	S ₄	1
0	S ₄	S ₂	1
1	S ₄	S ₃	0
0	S ₅	S ₂	1
1	S ₅	S ₅	0

Table Q7 (a)

- b. Explain modeling and assumption for retiming in sequential circuit optimization using network models. (10 Marks)
- 8 a. Explain integer linear programming model of scheduling with resource constraints. (10 Marks)
- b. Briefly explain rule based library binding. (10 Marks)
