

**M.Tech. Degree Examination, Dec.2014/Jan.2015**  
**Design of Analog and Mixed Mode VLSI Circuits**

Time: 3 hrs.

Max. Marks: 100

**Note: Answer any FIVE full questions.**

- 1 a. Derive and explain I/V characteristics of MOSFET. (12 Marks)  
 b. Explain the following second order effects of MOSFET: i) Body effect; ii) Channel length modulation. (08 Marks)
- 2 a. Explain common-source stage with resistive load and draw small signal model of common source stage including the transistor o/p resistance. (10 Marks)  
 b. Explain source follower with its input-output characteristics and also draw small signal equivalent circuit of source follower. (10 Marks)
- 3 a. Explain miller effect using Miller's theorem. (06 Marks)  
 b. Draw and explain high frequency model of a cascade stage. (08 Marks)  
 c. Neglecting channel-length modulation, compute the transfer function of the common-gate stage shown in Fig.Q.3(c). (06 Marks)

 


Fig.Q.3(c)

- 4 a. Explain differential pair with MOS loads and explain how voltage gain increased for the same. (08 Marks)  
 b. Explain cascade current mirrors. (12 Marks)
- 5 a. In the circuit of Fig.Q.5(a), assume the Op-Amp is a single-pole voltage amplifier. If  $V_{in}$  is a small step calculate the time required for the o/p voltage to reach within 1% of its final value. What unity-gain bandwidth must the op-amp provide if  $1 + R_1/R_2 \approx 10$  and the settling time is to be less than 5ns? For simplicity, assume the low-frequency gain is much greater than unity. (10 Marks)

 


Fig.Q.5(a)

- b. Explain folded cascade op-amp with cascade PMOS loads and determine the small signal voltage gain. (10 Marks)

- 6 a. Write a note on the performance parameters of voltage controlled oscillator. (10 Marks)
- b. What is PLL? Explain basic PLL topology with neat diagrams. (10 Marks)
  
- 7 a. Explain the following: i) Negative TC voltage ; ii) Positive TC voltage. (10 Marks)
- b. Explain switched capacitor integrator with neat diagrams. (10 Marks)
  
- 8 a. Explain DAC specification with figures. (10 Marks)
- b. Explain flash ADC architecture with the help of block diagram and principle of conversion with an example for 3 bits. (10 Marks)

\*\*\*\*\*