

M.Tech. Degree Examination, June/July 2013

Design of Analog and Mixed Mode VLSI Circuits

Time: 3 hrs.

Max. Marks:100

Note: Answer any FIVE full questions.

- 1 a. Derive and explain I/V characteristics of MOSFET from fundamental concept. (12 Marks)
- b. Plot the variation of gate to source and gate to drain capacitance as function of gate to source voltage in different regions of operations of a MOSFET. Give explanation for each region. (08 Marks)
- 2 a. Derive an expression for voltage gain and output resistance of common source stage with source degeneration $\lambda \neq 0$ and $r \neq 0$. (15 Marks)
- b. Calculate the voltage gain of the circuit shown in Fig.Q2(b). (05 Marks)

 


Fig.Q2(b)

- 3 a. Calculate the voltage gain of the circuit in Fig.Q3(a) if $\lambda \neq 0$ and $r \neq 0$.

 


Fig.Q3(a)

- b. Give the circuit of folded cascade stage with PMOS input transistor and obtain its large signal characteristics V_{out} versus V_{in} . (10 Marks)

- 4 a. Calculate the input resistance of the circuit shown in Fig.Q4(a).

 


Fig.Q4(a)

(06 Marks)

- 4 b. Obtain the high frequency model of a common source stage. Obtain its transfer function and discuss its frequency response. (14 Marks)

- 5 a. For the circuit shown in Fig.Q5(a), find:

- What is the required input CM for which R_{ss} sustains 0.5V?
- Calculate R_D for a differential gain of 5.
- What happens at the output, if the input CM level is 50 mV higher than the value calculated in (i)?

Assume: $\left(\frac{W}{L}\right)_{1,2} = \frac{25}{0.5}$, $\mu_{nCox} = 50\mu A/V^2$, $V_{Th} = 0.6 V$, $\lambda = r = 0$, $V_{DD} = 3V$,

Tail current = 1 mA, $R_{D1} = R_{D2} = R_D$

 


Fig.Q5(a)

- b. Explain the operation of Gilbert cell. (10 Marks)
- 6 a. What is VCO? Explain VCO. (04 Marks)
- b. Explain important performance parameters of VCO's. (08 Marks)
- c. A VCO sensor a small sinusoidal control voltage $V_{cont} = V_m \cos(\omega_m t)$. Determine the output waveform and its spectrum. (08 Marks)
- 7 a. Explain the operation of current steering DAC architecture with neat diagrams and equations. (10 Marks)
- b. Explain the operation of pipeline ADC architecture with neat diagrams and example. (10 Marks)
- 8 Write technical notes on the following:
- PLL as a frequency synthesizer. (10 Marks)
 - Resistor string DAC using binary switch array. (10 Marks)
