

USN

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

12EC025

**M.Tech. Degree Examination, June/July 2014**  
**Design of Analog and Mixed Mode VLSI Circuit**

Time: 3 hrs.

Max. Marks:100

**Note: Answer any FIVE full questions.**

- 1 a. Derive expression for the drain current in triode, deep triode and saturation region of MOSFET device. Also draw  $I_D/V_{DS}$  curves for these regions. (10 Marks)
- b. Show that the output voltage varies linearly with reference to input voltage in the case of a CS stage with diode connected load and source depection. (10 Marks)
- 2 a. Quantify the behavior of a mos differential pair as a function of input differential voltage. (08 Marks)
- b. In the circuit shown in Fig. 2(b)  $m_2$  is twice as wide as  $m_1$ . Calculate the small signal gain if the bias voltages of  $v_{in1}$  and  $v_{in2}$  core equal. (06 Marks)

 


Fig. Q 2(b)

- c. Calculate the small signal gain of the circuit shown in Fig. Q2(c). (06 Marks)

 


Fig. Q 2(c)

- 3 a. Derive expression for the input impedance of a source follower in low frequency and high frequency regions. (10 Marks)
- b. Derive transit function of a cascade stage. (10 Marks)
- 4 a. Draw the circuit diagram of a current mirror generating output current which is independent of supply voltage and explain its operation. Also derive expression for the output current. (08 Marks)
- b. Explain the effect of op amp off set voltage on the output voltage of bund gap reference and means to overcome the same. (06 Marks)
- c. What is the effect of channel charge injection on the output voltage in the case of switched capacitor circuits? Explain in detail. (06 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
 2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

- 5 a. Show that in a three stage ring oscillator, the minimum gain /stage =2 and  $\omega_{osc} = \sqrt{3} \omega_0$  for oscillations to set in where  $\omega_0 = 3\text{dB}$  bound width of each stage. (06 Marks)
- b. Draw the circuit diagram of a Colpitt oscillator and explain its operation. (06 Marks)
- c. A VCO senses a small sinusoidal control voltage  $V_{cont} = V_m \cos \omega_m t$ . Determine the output waveform and its spectrum. (08 Marks)
- 6 a. Explain the working of a simple PLL with necessary block diagrams, wave forms, frequency and phase relations. (10 Marks)
- b. Explain how frequency multiplication and synthesis are achieved using PLL concepts. (10 Marks)
- 7 a. Explain the working of S/H circuit with special reference to sample mode, hold mode and aperture error. (10 Marks)
- b. Explain the following specifications with reference to ADC :
- DNL
  - INL
  - Off set
  - Gain error
  - SNR. (10 Marks)
- 8 a. Explain R – ZR ladder network with necessary diagram and equations. (10 Marks)
- b. Explain the operation of a pipeline ADC architecture, with neat diagram, (10 Marks)

\* \* \* \* \*