

# CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

18EE62

## Sixth Semester B.E. Degree Examination, June/July 2024 Power System Analysis – I

Time: 3 hrs.

Max. Marks: 100

*Note: Answer any FIVE full questions, choosing ONE full question from each module.*

### Module-1

- 1 a. Show that per unit impedance of a transformer remains same whether it is referred to HV or LV winding. (08 Marks)
- b. Draw the per unit reactance diagram for the power system shown in Fig.Q1(b). The ratings of the various components are:

$G_1$  : 10 MVA, 6.6 KV,  $X'' = 0.1$  PU

$G_2$  : 20 MVA, 11.5 KV,  $X'' = 0.1$  PU

$T_1$  : 10 MVA, 3 phase, 6.6/115 KV,  $X = 0.15$  PU

$T_2$  : 3 single phase units each rated 10 MVA 7.5/75 KV,  $X = 0.1$  PU

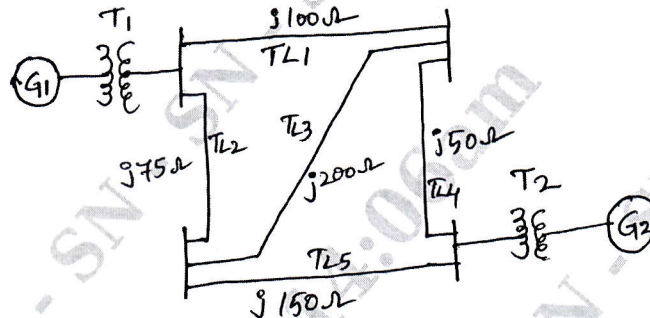


Fig.Q1(b)

Selecting generator 1 ratings as the base

(12 Marks)

OR

- 2 a. Define per unit quantity. Mention its advantages. (06 Marks)
- b. Draw the reactance diagram with all reactances marked in per unit. Choose a base of 50 MVA, 13.8 KV in the circuit of generator 1. For the system shown in Fig.Q2(b).

$G_1$  : 20 MVA, 13.8 KV,  $X'' = 0.20$  PU

$G_2$  : 30 MVA, 18 KV,  $X'' = 0.20$  PU

$G_3$  : 30 MVA, 20 KV,  $X'' = 0.20$  PU

$T_1$  : 25 MVA, 220 Y/13.8Δ KV,  $X = 10\%$

$T_2$  : Single phase units each rated 10 MVA, 127/18 KV,  $X = 10\%$

$T_3$  : 35 MVA, 220 Y/22 Y KV  $X = 10\%$

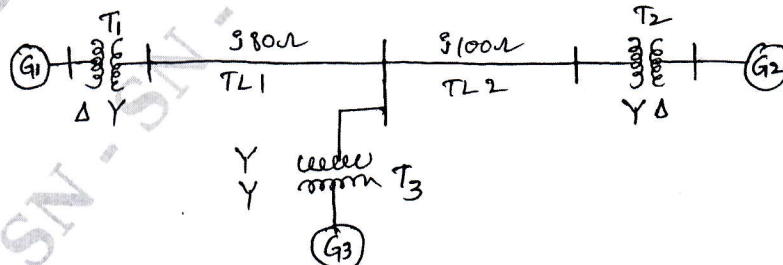


Fig.Q2(b)

(10 Marks)

- c. Mention the assumptions made while drawing the impedance diagram. (04 Marks)

**Module-2**

- 3 a. With the help of oscillogram of short circuit current of a synchronous generator operating at no load. Explain subtransient, transient and steady state periods. (10 Marks)
- b. Fig.Q3(b) shows a generating station, feeding 132 KV system. Determine fault current, fault level, fault currents supplied by generators for a 3 phase fault at the receiving end of the bus. The line is 200 km long. Take a base of 100 MVA, 11 KV on the generator circuit.

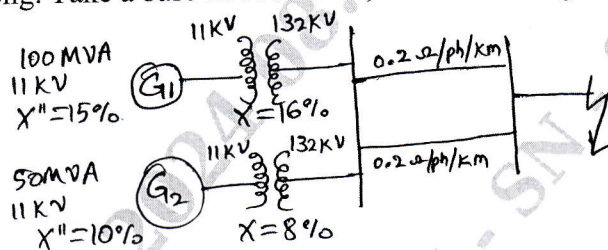


Fig.Q3(b)

(10 Marks)

**OR**

- 4 a. What is doubling effect in transmission line? Explain with suitable waveforms and diagram. (10 Marks)
- b. A 75000 KVA, 6.6 KV generator connected through a 5 cycle breaker has reactance  $X_d'' = 9\%$ ,  $X_d' = 15\%$  and  $X_d = 100\%$ . It is operating at no load and at rated terminal voltage, when a short circuit occurs beyond the circuit breaker. Find:
- Sustained short circuit current
  - Initial symmetrical rms current
  - Maximum possible DC offset current after 5 cycles
  - Making capacity required
  - Braking capacity required
  - Interrupting MVA

(10 Marks)

**Module-3**

- 5 a. Define symmetrical components. Resolve an unbalanced 3 phase voltages of a power system into the symmetrical components and also in vice versa. (08 Marks)
- b. The line to neutral voltage in a 3 phase system are  $V_{an} = 200 \angle 0^\circ$  V,  $V_{bn} = 200 \angle 100^\circ$  V and  $V_{cn} = 400 \angle 270^\circ$  V. Find symmetrical components of the voltages. (06 Marks)
- c. Draw the zero sequence impedance networks of a transformer for the following connections:
- $Y_{\pm} - Y$
  - $\Delta - Y_{\pm}$
  - $\Delta - \Delta$

(06 Marks)

**OR**

- 6 a. What are sequence impedances and networks? Explain sequence impedances and networks of synchronous generator. (10 Marks)
- d. Draw positive, negative and zero sequence networks for the power system shown in Fig.Q6(b). Choose a base of 50 MVA, 220 KV in the 50Ω transmission line.

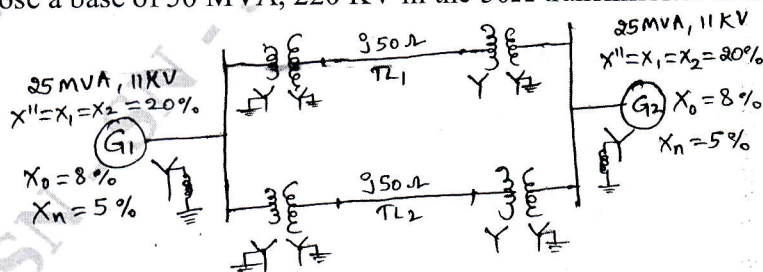


Fig.Q6(b)

Assume transmission line  $X_0 = 250\%$  of  $X_1$ .Three transformers (each) : 20 MVA, 11 Y/220Y KV,  $X = 15\%$ .

(10 Marks)



**Module-4**

- 7 a. Derive an expression for single line to ground (SLG) fault through impedance ( $Z_f$ ) in a power system. Show the interconnection of sequence networks. (08 Marks)
- b. A synchronous motor is receiving power of 10 MW at 0.8 PF lagging at a voltage of 6 KV as shown in Fig.Q7(b). A SLG fault occurs at the middle of the transmission line through fault reactance of  $5 \Omega$ . Determine the fault current. The ratings of the apparatus are:
- G : 20 MVA, 11 KV,  $X_1 = 0.2$  PU,  $X_2 = X_0 = 0.1$  PU  
 $T_1$  : 18 MVA, 11.5/34.5 KV,  $X_1 = X_2 = X_0 = 0.1$  PU,  $X_n = 0.066$  PU  
 $T_2$  : 15 MVA, 34.5/6.9 KV,  $X_1 = X_2 = X_0 = 0.1$  PU  
 Motor : 15 MVA, 6.9 KV,  $X_1 = 0.2$  PU,  $X_2 = X_0 = 0.1$  PU,  $X_n = 0.066$  PU  
 Tr. Line :  $X_1 = X_2 = 5 \Omega$ ,  $X_0 = 20 \Omega$   
 Choose 20 MVA, 11 KV on G circuit.

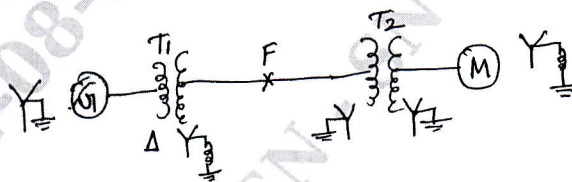


Fig.Q7(b)

(12 Marks)

**OR**

- 8 a. Discuss one conductor and two conductor open faults. (10 Marks)
- b. Derive an expression for fault current when line to line (LL) fault occurs in a power system through fault impedance. (10 Marks)

**Module-5**

- 9 a. Explain the classification of power system stability. (08 Marks)
- b. Derive the expression for swing equation. (06 Marks)
- c. A 60 Hz, 4 pole turbo-generator rated 500 MVA, 22 KV has an inertia constant  $H = 7.5$  MW-sec/MVA. Find:
- Kinetic energy stored in the rotor at the synchronous speed.
  - The angular acceleration, if electrical power developed is 400 MW, when the input less rotational losses is 740000 HP
  - Moment of inertia
  - Inertia constant  $M$  and angular acceleration

(06 Marks)

**OR**

- 10 a. Explain the concept of equal area criterion when a power system is subjected to sudden increase in load. (08 Marks)
- b. Write short note on critical clearing angle and critical clearing time. (06 Marks)
- c. Mention the factors affecting transient stability. (06 Marks)

\*\*\*\*\*