

--	--	--	--	--	--	--	--	--	--

**Third Semester B.E. Degree Examination, Dec.2024/Jan.2025**  
**Analog and Digital Electronics**

Time: 3 hrs.

Max. Marks: 100

*Note: Answer any FIVE full questions, choosing ONE full question from each module.*

**Module-1**

- 1 a. Explain the construction, working and V-I characteristics of photo diode. (06 Marks)  
 b. List the different types of BJT biasing. Derive the expression for fixed bias circuit. (06 Marks)  
 c. With the help of neat circuit diagram and waveform explain the working principle of relaxation oscillator. (08 Marks)

**OR**

- 2 a. With a neat waveform and circuit diagram, explain the working of monostable multivibrator. (06 Marks)  
 b. Explain the working of R-2R ladder D to A converter. (06 Marks)  
 c. Explain performance parameters of a power supply. (08 Marks)

**Module-2**

- 3 a. A logic circuit realizing the function  $f$  has four inputs A, B, C and D. The three inputs A, B and C are the binary representation of the digits 0 through 7 with A being the most significant bit. The input D is an odd parity bit, i.e., the value of D is such that A, B, C and D always contain an odd number of 1's. (For example, the digit 1 is represented by ABC = 001 and D = 0, and the digit 3 is represented by ABCD = 0111). The function  $f$  has value 1 if the input digit is an odd number and value 0 if the input digit is an even number.  
 i) List the minterms and don't-care minterms of  $f$  in algebraic form.  
 ii) List the maxterms and don't-care maxterms of  $f$  in algebraic form. (10 Marks)  
 b. Solve for the Boolean expression using K-map to get minimum SOP and minimum POS expression:  
 i)  $f(A, B, C, D) = \sum m(0, 1, 4, 8, 9, 10) + d(2, 11)$   
 ii)  $f(A, B, C, D) = \pi M(0, 1, 3, 4, 7)$  (10 Marks)

**OR**

- 4 a. Determine the essential prime implicants using Q method for the function  $f(A, B, C, D) = \sum m(0, 1, 2, 3, 10, 12, 11, 13, 14, 15)$ . (10 Marks)  
 b. Explain with explain Petrik's method. (06 Marks)  
 c. Find the minimum SOP for the function  $f(A, B, C) = \sum m(2, 6, 7)$  using Quine McCluskey method. (04 Marks)

**Module-3**

- 5 a. How do you detect static hazards in combinational logic circuits? Explain with examples. (06 Marks)  
 b. With a neat diagram, explain 3 to 8 line decoder. (06 Marks)  
 c. Design 7 segment decoder and realize using PLA. (08 Marks)

OR

- 6 a. Implement  $Y(A, B, C, D) = \sum m(0, 2, 3, 4, 5, 8, 9, 10, 11, 12, 13, 15)$  using 16 – to – 1 multiplexer (IC 74150) and 8 – to – 1 multiplexer. (08 Marks)  
 b. Implement full adder using PAL. (08 Marks)  
 c. Explain simulation and testing of digital circuits. (04 Marks)

**Module-4**

- 7 a. Explain the structure of VHDL program. Write VHDL code for 4-bit parallel adder using full adder as component. (08 Marks)  
 b. Construct SR latch using NAND gates and derive the characteristics equation for the same. (08 Marks)  
 c. Differentiate between latch and flip flop. Show how SR flip flop can be converted to D flip flop. (04 Marks)

OR

- 8 a. Derive the characteristics equations for D, T, SR and JK flipflops. (08 Marks)  
 b. Explain the working of a JK flip flop. Write its Truth table, state diagram and excitation table. (08 Marks)  
 c. Give the implementation of T flip flop from D flip flop. (04 Marks)

**Module-5**

- 9 a. What is register? Explain how 4 bit register with data, load, clear and clock input is constructed using D flip-flops. (06 Marks)  
 b. With a neat diagram, explain 4 bit SISO register. (06 Marks)  
 c. Design a random counter using T flip flops whose transition graph is shown in Fig.Q.9(c).

 


Fig.Q.9(c)

(08 Marks)

OR

- 10 a. With the help of state graph, state and transistor tables and timing diagrams explain sequential parity checker. (08 Marks)  
 b. Differentiate between Moore and Melay machines. Analyze following Moore sequential circuit for an input sequence of  $X = 01101$  and draw the timing diagram. (08 Marks)  
 c. Write a note on Ring counter. (04 Marks)

\* \* \* \* \*