

--	--	--	--	--	--	--	--	--	--

Third Semester B.E./B.Tech. Degree Examination, Dec.2024/Jan.2025



Digital Logic Circuits

Time: 3 hrs.

Max. Marks: 100

Note: 1. Answer any FIVE full questions, choosing ONE full question from each module.
2. M : Marks , L: Bloom's level , C: Course outcomes.

Module – 1				M	L	C
Q.1	a.	Define combinational logic. What are Canonical forms in combinational logic? Explain the difference between SOP and POS canonical forms with suitable examples.		05	L1	CO1
	b.	What are prime implicant and essential prime implicant? Simplify the given Boolean function using KMap and identify its PI and EPI. $f(a,b,c,d) = \sum_m(0,1,2,5,6,7,8,9,10,13,14,15)$		08	L2	CO1
	c.	Given $f(a,b,c) = \bar{a}b + ac + \bar{b}c$. Express it in canonical SOP and canonical POS.		07	L2	CO1
OR						
Q.2	a.	Minimize the following expression in POS using K-map: $f(a,b,c,d) = \sum m(1,3,7,11,15) + \sum d(0,2,5)$		05	L3	CO1
	b.	Simplify the Boolean expression using K-map. $f(p,q,r,s,t) = \sum m(0,2,4,6,8,16,18,28,30) + dc(3,7,11,19,27,31)$		05	L3	CO1
	c.	Using Quine McCluskey and PI Reduction Table, determine minimal SOP for the function, $f(w,x,y,z) = \sum m(1,3,4,7,8,9,12,14) + \sum dc(2,13)$		10	L3	CO1
Module – 2						
Q.3	a.	Write the Truth table for 8 line to 3 line priority Encoder.		04	L2	CO2
	b.	Write short note on look ahead carry adder.		06	L2	CO2
	c.	Design a combinational circuit to convert BCD to Excess 3 code.		10	L3	CO2
OR						
Q.4	a.	Design full adder using a decoder (74138).		05	L3	CO2
	b.	Implement the following function using 8 : 1 MUX. Treat w, x, y as select lines, $f(w,x,y,z) = \sum m(0,1,5,6,7,9,10,15)$.		05	L3	CO2
	c.	Implement 2 bit comparator using 4-16 decoder.		10	L3	CO2
Module – 3						
Q.5	a.	With the help of logic diagram, explain the working of Master Slave JK flipflop and explain how race around condition is eliminated.		10	L2	CO3
	b.	Explain how SR flip flop/latch act as switch debouncing circuit and draw its waveform.		06	L2	CO3
	c.	Differentiate between latch and flip flop.		04	L2	CO3
OR						
Q.6	a.	Derive the characteristics equation of SR, JK and T flip flop.		06	L3	CO3
	b.	With a logic diagram, explain the working of SR-flip flop.		07	L2	CO3
	c.	With the help of logic diagram, explain the working of positive edge Triggered D-flip flop.		07	L2	CO3

  Module – 4																													
Q.7	a.	Design a synchronous counter for the following sequence using JK flip flop.	10	L3	CO4																								
<div></div>			Fig. Q7 (a)																										
	b.	Design synchronous MOD-6 counter using clocked T flip flop.	10	L3	CO4																								
OR																													
Q.8	a.	Design 4 bit register using positive edge triggered DFF to operate as below :	12	L4	CO4																								
		<table><tr><th>Mode</th><th>Select</th><th></th><th>Register operation</th></tr><tr><td>A₁</td><td>A₀</td><td></td><td></td></tr><tr><td>0</td><td>0</td><td>→</td><td>Hold</td></tr><tr><td>0</td><td>1</td><td>→</td><td>Shift Right</td></tr><tr><td>1</td><td>0</td><td>→</td><td>Shift Left</td></tr><tr><td>1</td><td>1</td><td>→</td><td>Parallel load</td></tr></table>	Mode	Select		Register operation	A ₁	A ₀			0	0	→	Hold	0	1	→	Shift Right	1	0	→	Shift Left	1	1	→	Parallel load			
Mode	Select		Register operation																										
A ₁	A ₀																												
0	0	→	Hold																										
0	1	→	Shift Right																										
1	0	→	Shift Left																										
1	1	→	Parallel load																										
	b.	Explain 4 bit SISO uni-directional shift register using DFF (Consider positive edge triggered).	08	L2	CO4																								
Module – 5																													
Q.9	a.	Design a sequential circuit using TFF for the figure shown in Fig. Q9 (a).	12	L3	CO5																								
<div></div>			Fig. Q9 (a)																										
	b.	With a neat diagram, explain mealy and Moore model in a sequential circuit analysis.	08	L2	CO4																								
OR																													
Q.10	a.	Write short note on : (i) Read / write memories (ii) Programmable ROM	10	L2	CO6																								
	b.	Write short note on : (i) Flash memory (ii) EPROM	10	L2	CO6																								
