

CBCS SCHEME

USN

BEE302

Third Semester B.E./B.Tech. Degree Examination, Dec.2024/Jan.2025




Electric Circuit Analysis

Time: 3 hrs.

Max. Marks: 100


Note: 1. Answer any FIVE full questions, choosing ONE full question from each module.

2. M : Marks , L: Bloom's level , C: Course outcomes.

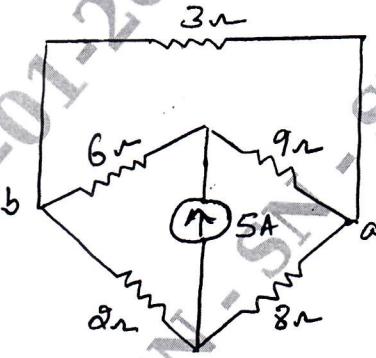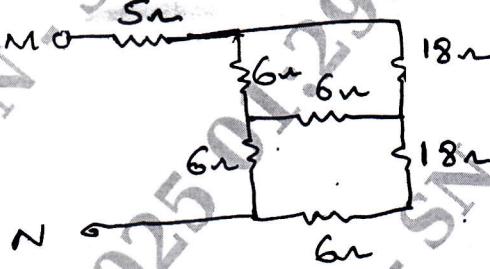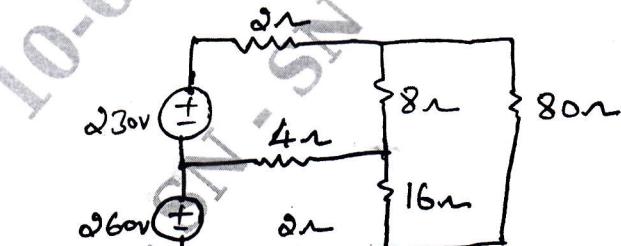Module - 1			M	L	C
Q.1	a.	<p>Use source mobility of sources transformation to reduce the given network, shown in Fig Q1(a) into a single voltage source in series with a resistor between points a b.</p>  <p>Fig Q1(a)</p>	6	L3	CO1
	b.	<p>Determine the equivalent resistance between the terminals MN for the networks shown in Fig Q1(b).</p>  <p>Fig Q1(b)</p>	6	L3	CO1
	c.	<p>Use Mesh current analysis to find the power dissipated in the 80Ω resistor of circuit shown in Fig Q1(c).</p>  <p>Fig Q1(c)</p>	8	L3	CO1


OR

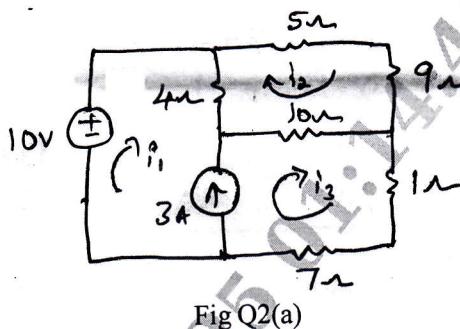- Q.2** a. Determine the circuit i_1 , i_2 , and i_3 in the circuit of Fig Q2(a), using mesh current method.




6 L3 CO1

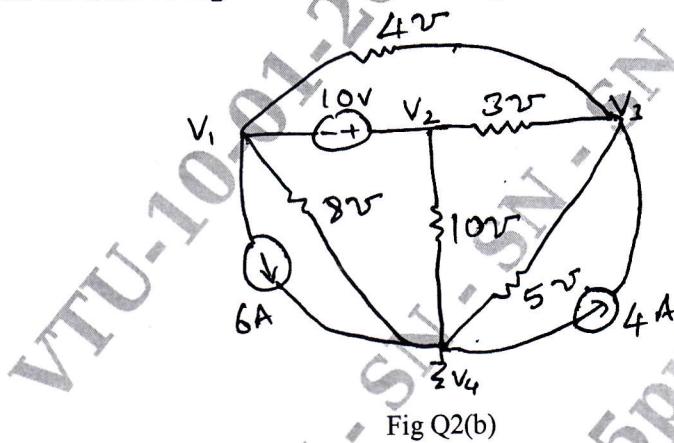- b. Find the node voltages for the circuit of Fig Q2(b), using nodal analysis.



8 L3 CO2

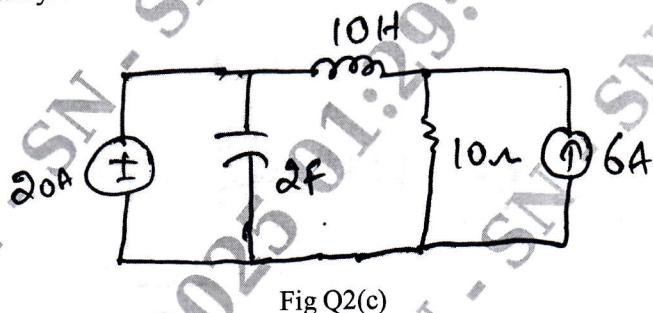- c. Define Duality. Draw the dual of the network shown in Fig Q2(c).




6 L3 CO1

Module - 2




- Q.3** a. State and prove super position theorem.

8 L1 CO2



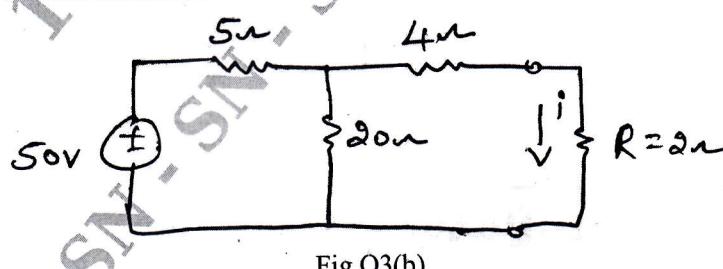
- b. For the network shown in Fig Q3(b), find the current i though $R = 2\Omega$ using the Thevenin's theorem.



6 L3 CO2

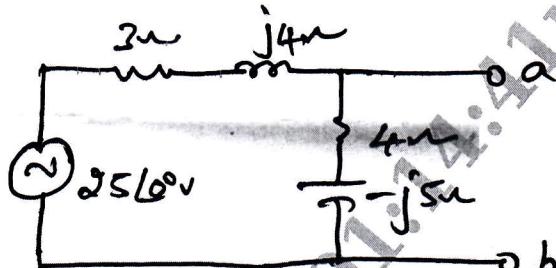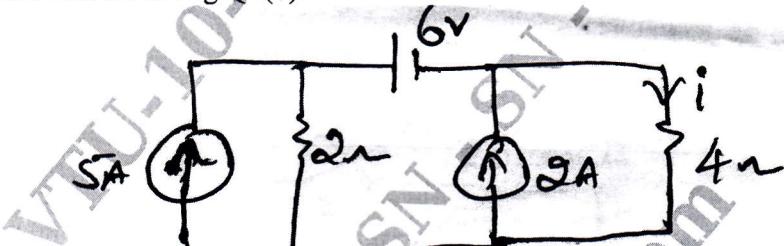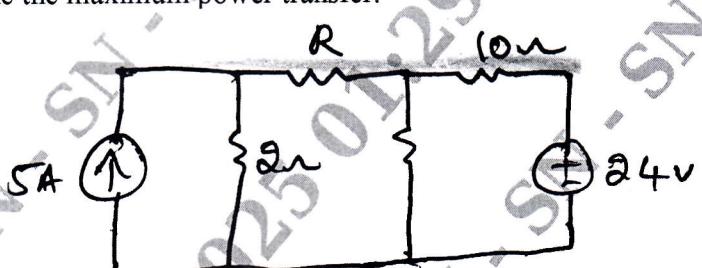	c.	Obtain the Norton's equivalent for the circuit shown in Fig Q3(c), between point a of b.	6	L3	CO2
					
Fig Q3(c)					
		OR			
Q.4	a.	State and explain maximum power transfer theorem for DC circuit (Resistive Load).	6	L1	CO2
	b.	Find the current through 4Ω resistor using super position theorem for the circuit shown in Fig Q4(b).	8	L3	CO2
					
		Fig Q4(b)			
	c.	Determine the value of R for the circuit shown in Fig Q4(c) and also determine the maximum power transfer.	6	L3	CO2
					
		Fig Q4(c)			
Module - 3					
Q.5	a.	Explain with circuit diagram how to determine of resonant frequency, bandwidth and Q of a series circuit.	10	L2	CO2
	b.	For the network elements R, L and C, write the equivalent circuit $A + t = 0^+$ [initial condition] $A + t = \infty$ [find condition]	4	L2	CO4
	c.	A series RLC circuit has $R = 4\Omega$, $L = 1\text{mH}$ an $C = 10\mu\text{F}$, calculate Q-factor, bandwidth, resonant frequency and half frequencies.	6	L3	CO2

OR

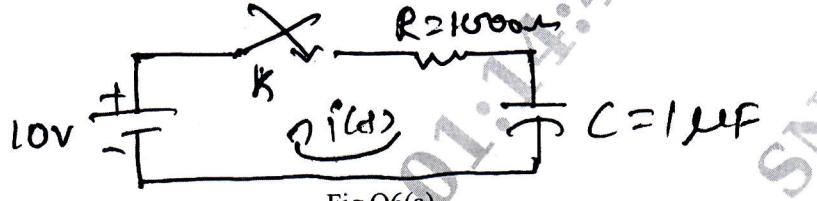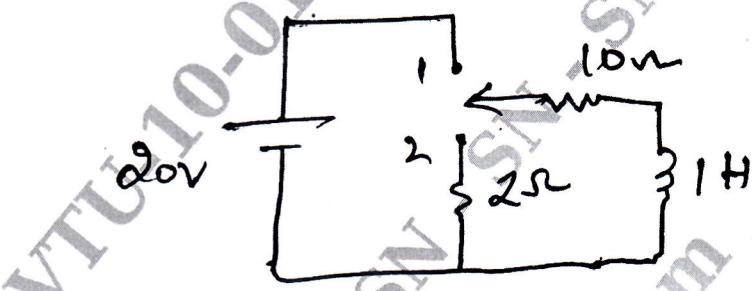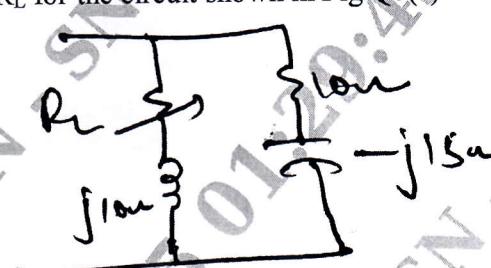Q.6	a.	In the network shown in Fig Q6(a), the switch K is closed at $t = 0$ with the capacitor uncharged. Find the values for i , di/dt and d^2i/dt^2 at $t = 0^+$.	8	L3	CO4
					
	b.	Determine di/dt and d^2i/dt^2 at $t = 0^+$, when the switch K is moved from position 1 to 2 at $t = 0$ for the Fig Q6(b) shown steady state having reached before switching.	8	L3	CO4
					
	c.	Find the value of R_L for the circuit shown in Fig Q6(c)	4	L3	CO
					




Module - 4

Q.7	a.	State and prove initial and final Value theorem.	10	L1	CO5
	b.	Find the laplace transform of the following : i) $\sin wt$ ii) $\cos wt$ iii) $e^{-at} \sin wt$ iv) $e^{-at} \cos wt$.	10	L2	CO5

OR

Q.8	a.	Obtain the Laplace transform of i) $u(t)$ ii) $r(t)$ iii) $\delta(t)$.	10	L2	CO5
	b.	Apply the initial value and find and final value theorem respectively to the S-domain equation of $I_1(s)t$ of $I_2(s)$ given i) $I_1(s) = \frac{6.67(s+250)}{s(s+166.7)}$ ii) $I_2(s) = \frac{6.67}{s+166.7}$	10	L2	CO5

Module - 5

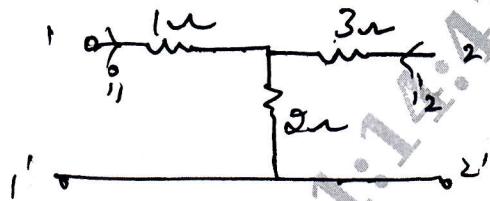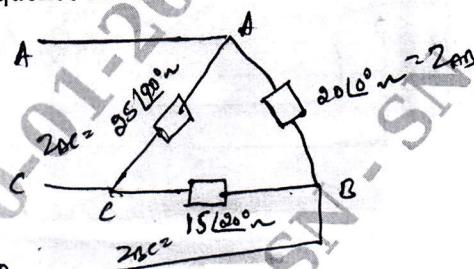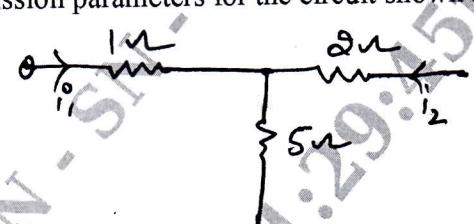Q.9	a.	Determine the z-parameter of y-parameter for the circuit shown in Fig Q9(a).	10	L3	CO3
					
	b.	A 3φ supply with line voltage of 250V has an unbalanced delta connected load as shown in Fig Q9(b). Determine line currents active and reactive power for phase sequence ABC.	10	L3	CO3
					
Q.10	OR		10	L3	CO3
	a.	Find the transmission parameters for the circuit shown in Fig Q10(a)			
					
b.	3φ, 4-wire 208V CBA system as shown in Fig Q10(b) has a star connected load with $Z_A = 5[0^\circ] \Omega$, $Z_B = [30^\circ] \Omega$ and $Z_C = 10[-60^\circ] \Omega$. Obtain the phase current, line currents and current through neutral wire.	10	L3	CO3	
					