





Third Semester B.E./B.Tech. Degree Examination, June/July 2024

Electric Circuit Analysis

Time: 3 hrs.



Max. Marks: 100

- Note: 1. Answer any FIVE full questions, choosing ONE full question from each module.*
 2. VTU Formula Hand Book is permitted.
 3. M : Marks , L: Bloom's level , C: Course outcomes.

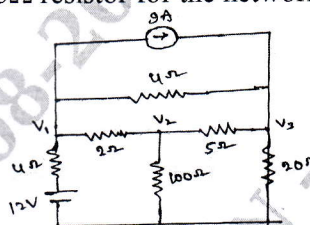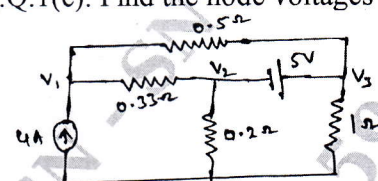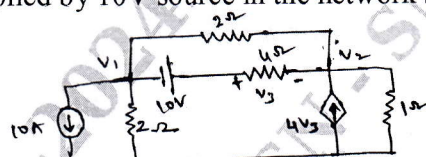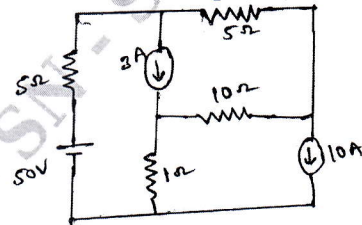
Module – 1				M	L	C
Q.1	a.	Explain active and passive elements with example.		4	L2	CO1
	b.	Find the voltage across 5Ω resistor for the network shown in Fig.Q.1(b).		8	L3	CO1
 <p style="text-align: center;">Fig.Q.1(b)</p>						
	c.	In the network of Fig.Q.1(c). Find the node voltages V_1 , V_2 and V_3 .		8	L3	CO1
 <p style="text-align: center;">Fig.Q.1(c)</p>						
OR						
Q.2	a.	Derive the relationship between Δ - Y transformation.		5	L2	CO1
	b.	Find the power supplied by 10V source in the network shown in Fig.Q.2(b).		7	L3	CO1
 <p style="text-align: center;">Fig.Q.2(b)</p>						
	c.	Determine the power delivered by the voltage source and the current in the 10Ω resistor of the network shown in Fig.Q.2(c).		8	L3	CO1
 <p style="text-align: center;">Fig.Q.2(c)</p>						

1 of 4


Module – 2

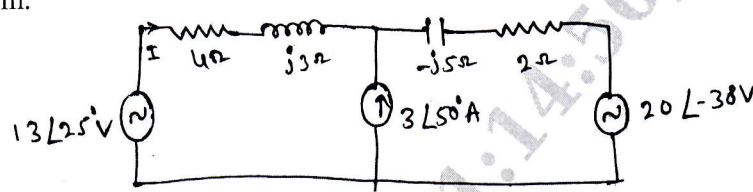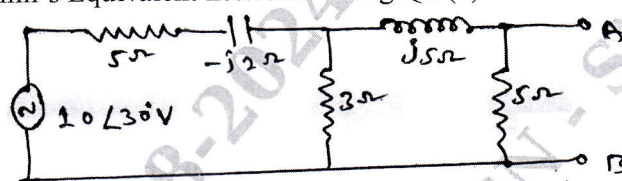Q.3	a.	Find the current I in the network shown in Fig.Q.3(a) using superposition theorem.	10	L3	CO2
		 <p>Fig.Q.3(a)</p>			
	b.	Find Thevenin's Equivalent network for Fig.Q.3(b)	10	L3	CO2
		 <p>Fig.Q.3(b)</p>			

OR

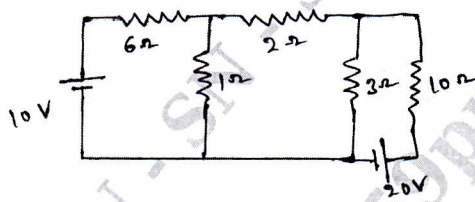Q.4	a.	Find the current through the 10Ω resistor for the Fig.Q.4(a) using Norton's theorem.	10	L3	CO2
		 <p>Fig.Q.4(a)</p>			
	b.	State and prove maximum power transfer theorem.	10	L2	CO2


Module – 3

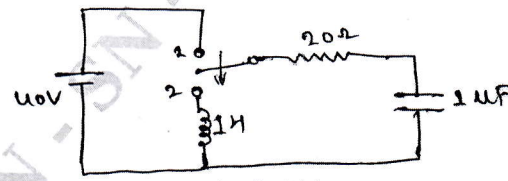Q.5	a.	A series RLC circuit has $R = 10\Omega$ and $L = 60\text{mH}$. At a frequency of 25Hz the power factor of the circuit is 45° lead. At what frequency will the circuit be resonant.	5	L3	CO3
	b.	What are initial conditions? show the behavior of R, L and C elements at the time of switching at $t = 0$ both at $t = 0^+$ and $t = \infty$.	8	L2	CO3
	c.	For a network shown in Fig.Q.5(c) switch is changed from the position 1 to the position 2 at $t = 0$. Steady state condition reached before switching. Find the values i , $\frac{\partial i}{\partial t}$ and $\frac{\partial^2 i}{\partial t^2}$ at $t = 0^+$.	7	L4	CO3
		 <p>Fig.Q.5(c)</p>			



OR

Q.6	a.	Derive an expression for R – C circuit under DC excitation find voltage across R and C also.	10	L2	CO3
	b.	A series resonant circuit has an impedance of 500Ω at resonant frequency. Cut off frequencies are 10kHz and 100Hz. Determine: i) Resonant frequency ii) Value of L and C iii) Quality factor at resonant frequency.	10	L3	CO3


Module – 4

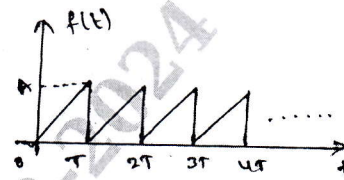Q.7	a.	Find the Laplace transform of the waveform shown in Fig.Q.7(a).	8	L4	CO4
		 <p>Fig.Q.7(a)</p>			
	b.	Verify the initial and final value theorems for $f(t) = e^{-t}(t+1)^2$.	4	L3	CO4
	c.	State and prove initial value theorem.	8	L2	CO4

OR

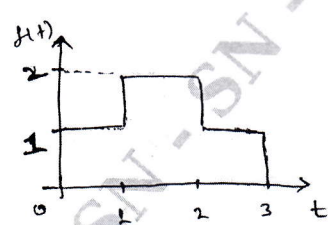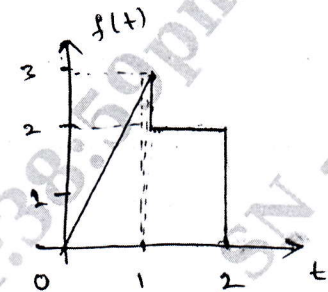Q.8	a.	Find the Laplace transform of the waveform given below in Fig.Q.8(a) and (b) respectively.	10	L4	CO4
		 <p>Fig.Q.8(a)</p>  <p>Fig.Q.8(b)</p>			
	b.	Find the Laplace transform of a unit step. Unit impulse and unit ramp functions.	10	L3	CO4

Module – 5

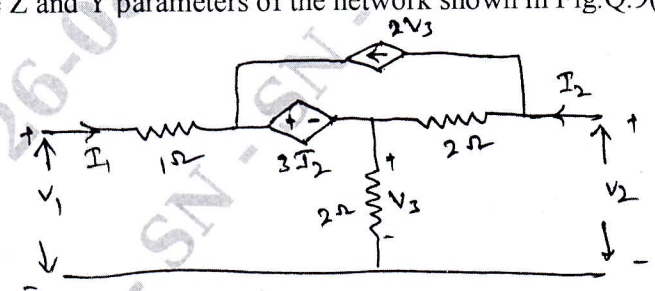Q.9	a.	Determine Z and Y parameters of the network shown in Fig.Q.9(a).	10	L4	CO5
		 <p>Fig.Q.9(a).</p>			
	b.	Express the Y-Parameters in terms of Z-Parameters.	10	L3	CO5

OR

Q.10 a. Obtain the ABCD parameters for the network shown in the Fig.Q.10(a).

10

L4

CO5

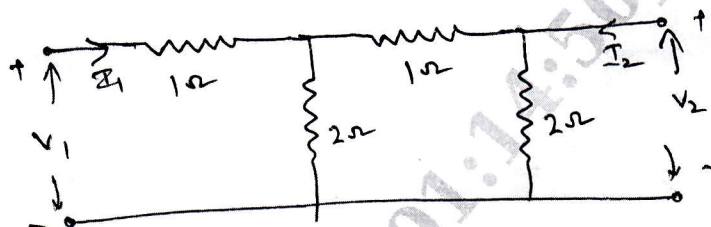


Fig.Q.10(a)

b. A 3-phase, 4-wire, 208V, CBA system as shown in Fig.Q.10(b) has star connected load with $Z_A = 5 \angle 0^\circ \Omega$, $Z_B = 5 \angle 30^\circ \Omega$, $Z_C = 10 \angle -60^\circ \Omega$. Obtain the phase current, line currents and current through neutral wire.

10

L4

CO5

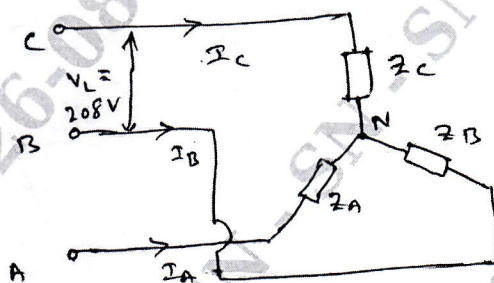


Fig.Q.10(b)
