


M.Tech. Degree Examination, Dec.09/Jan.10
Digital Circuits & Logic Design

Max. Marks:100

Time: 3 hrs.

Note: Answer any FIVE full questions.

 - 1 a. Explain the concept of threshold logic. (05 Marks)
b. Determine the function $f(x_1, x_2, x_3, x_4)$ realized by the network shown in Fig.1(b). (06 Marks)



- c. Given the switching function $f(x_1, x_2, x_3, x_4) = \Sigma(2, 3, 6, 7, 10, 12, 14, 15)$. Find a minimal threshold logic realization. (09 Marks)

- 2 a. For the circuit shown in Fig.2(a), wires m, n, p & q may become either s-a-0 or s-a-1. Determine a minimal fault-detection experiment by means of fault table. (10 Marks)

 


Fig.2(a)

 


Fig.3(a)

- Fig.2(a)
- b. What are critical and sub-critical errors? Determine the same for AND, OR, NAND, NOR & EX-OR gates. (05 Marks)
- c. With a net diagram, explain the basic structure of a quadded network. (05 Marks)
- 3 a. For the circuit shown in Fig.3(a), find all tests to detect the faults x_3 , s-a-0 & x_3 s-a-1. (10 Marks)
- b. Use the map method to find a minimal set of tests for multiple faults for the two-level AND-OR realization of the function
- $$f(w, x, y, z) = w\bar{z} + x\bar{y} + \bar{w}x + w\bar{x}y$$
- (10 Marks)
- 4 a. For the m/c shown in Table 4(a), find the equivalence partition and a corresponding reduced m/c in standard form. (10 Marks)
- | | NS | Z |
|----|----|---|
| NS | | |
| Z | | |

P.S.	NS, Z	
	x = 0	x = 1
A	F, 0	B, 1
B	G, 0	A, 1
C	B, 0	C, 1
D	C, 0	B, 1
E	D, 0	A, 1
F	E, 1	F, 1
G	E, 1	G, 1

Table 4(a)

- b. Draw the merger graph and compatibility graph and determine the minimal closed covering for the m/c shown in Table 4(b). (10 Marks)

Table 4(b)

P.S.	NS, Z			
	I ₁	I ₂	I ₃	I ₄
A	-	-	E, 1	-
B	C, 0	A, 1	B, 0	-
C	C, 0	D, 1	-	A, 0
D	-	E, 1	B, -	-
E	B, 0	-	C, -	B, 0

- 5 a. The m/c shown in Table 5(a) has the following closed partitions. $\pi_1 = \{\overline{ACE}; \overline{BDF}\}$, $\pi_2 = \{\overline{AF}; \overline{BE}; \overline{CD}\}$.
- i) Find a state assignment which reduces the interdependencies of the state variables.
- ii) Derive the logical equations and show the circuit diagram when unit delays are used as memory elements. (10 Marks)

Table 5(a)

P.S.	NS		Z
	x = 0	x = 1	
A	D	C	1
B	A	D	0
C	B	E	0
D	E	B	0
E	F	C	0
F	C	D	0

- b. For the m/c shown in Table 5(b) find the π -lattice. (10 Marks)

Table 5(b)

P.S.	NS	
	x = 0	x = 1
A	D, 0	C, 0
B	C, 0	D, 1
C	E, 0	F, 0
D	F, 0	F, 1
E	G, 0	H, 0
F	H, 0	G, 1
G	B, 0	A, 0
H	A, 0	B, 1

6 a.

Table 6(a)

P.S.	NS		Z	
	x = 0	x = 1	x = 0	x = 1
A	D	B	0	0
B	A	C	1	0
C	B	E	1	0
D	F	A	0	1
E	F	C	0	0
F	E	D	0	1

 


Fig.6(a)

- i) Determine state assignment for the m/c shown in Table 6(a) so that it will have the structure shown in Fig.6(a).
- ii) Show the state diagram of the input-independent component. (10 Marks)

P.S	NS			Z
	x ₁ x ₂	01	10	
A	C	B	D	0
B	A	E	C	0
C	E	B	D	0
D	C	C	E	0
E	E	D	B	1

Table 6(b)

Determine the set of all Mm pairs for the machine shown in Table 6(b)

(10 Marks)

- 7 a. For the m/c shown in Table 7(a), determine the synchronizing tree and synchronizing sequence to synchronize the m/c to state D. (10 Marks)

Table 7(a)

P.S.	NS, Z	
	x = 0	x = 1
A	B, 0	D, 0
B	A, 0	B, 0
C	D, 1	A, 0
D	D, 1	C, 0

- b. For the m/c shown in Table 7(b) construct the distinguishing tree. Obtain all possible distinguishing sequences. Write the response of m/c to the sequence 111. (10 Marks)

Table 7(b)

P.S.	NS, Z	
	x = 0	x = 1
A	C, 0	D, 1
B	C, 0	A, 1
C	A, 1	B, 0
D	B, 0	C, 1

- 8 a. Identify the m/c which is known to have two states and its response to the i/p sequence X is the o/p sequence Z, as shown below:

Time :	t ₁	t ₂	t ₃	t ₄	t ₅	t ₆	t ₇	t ₈
X :	1	1	1	0	1	0	1	
Z :	0	1	0	0	1	0	0	

(10 Marks)

- b. What is a diagnosable sequential m/c? Construct testing table and graph for the m/c shown in Table 8(b). (10 Marks)

Table 8(b)

P.S.	NS, Z	
	x = 0	x = 1
A	B, 0	D, 0
B	A, 0	B, 0
C	D, 1	A, 0
D	D, 1	C, 0
